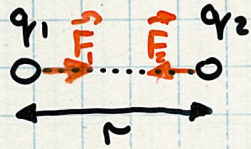


# Basic physical concepts

## Charge



$$F = k \frac{q_1 q_2}{r^2} \quad k = 9.0 \times 10^9 \text{ N m}^2 \text{ C}^{-2}$$

Coulomb's Law

1 C = a very large charge

$$\bar{e} = -1.6 \times 10^{-19} \text{ C}$$

↑ a historical convention



## Current

= movement of charge,  $I = \frac{dq}{dt}$

1 A = 1 C/s, by definition

DC = direct current; entirely concerned with BULK movement of electrons

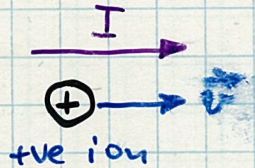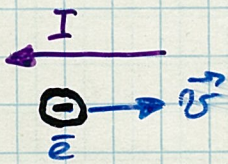Note: electric current opposite to movement of  $\bar{e}$ 's



Metals: a "sea" of free electrons moving in a crystal lattice, accelerated by voltage, impeded by collisions

Cu:  $8.5 \times 10^{22} \bar{e}/\text{cm}^3 \Rightarrow$  electrons in a metal need to move very little to create a large flow of charge, a large current

Ex:

- thermal motion of  $\bar{e}$  @ room temp.:  $\sim 10^5 \frac{\text{m}}{\text{s}}$
- drift velocity due to  $I = 1 \text{ A}$ :  $\sim 10^{-5} \frac{\text{m}}{\text{s}}$

Ex Calculate how many  $\bar{e}$ 's flow per second past a fixed point in a <sup>copper</sup> wire carrying 1A of current.

If the current moves from left to right, which way do the electrons move?

Ex How fast does the  $\bar{e}$  cloud in the wire ( $1\text{mm}^2$  cross-section) have to move to produce the current of 1A?

**Voltage** = energy (work) involved in moving charge

$V \equiv \frac{W}{q}$  (with green arrows pointing to 'work' and 'voltage'),  $1V = 1J/C$  (with green arrow pointing to 'Volt')

Also,  $\frac{d}{dt} W = \text{power} = V \frac{dq}{dt} = VI$ , for  $V = \text{const}$   
or  $1W = 1V \times 1A$  (with green arrow pointing to 'Watt')

Capitalize A, V, W → mA, μV, MW


Def-n of voltage requires a reference point (i.e. moving charge from where?) ⇒ concept of

**Ground** ↓


- Other names for voltage:
- "potential" (w.r.t. ground)
  - "potential difference" (between two points)
  - "electromotive force", emf

Analogy with water flow

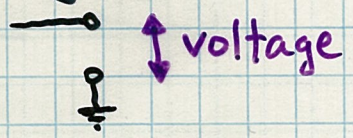charge, C  
 current,  $Cs^{-1} = A$   
 voltage,  $V = JC^{-1}$



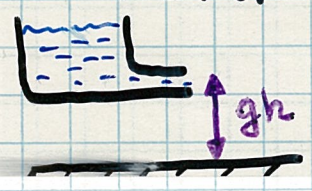Mass, kg  
 Mass flow,  $kg s^{-1}$   
 P.E. (per unit mass),  $J/kg$




# RESISTANCE

Drift velocity of charges in a conductor is limited by "frictional" effects:

$$I = \frac{V}{R}$$

$$\Rightarrow R = \frac{V}{I}$$

Ohm's Law.

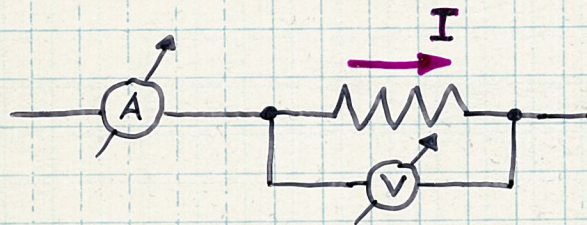

$$1 \Omega = \frac{1V}{1A}$$

Resistance is a property of the conducting material.

$$R = \rho L/A$$

$L$  = length


$A$  = cross-sectional area

$\rho$  = resistivity

Ex. Ag:  $\rho = 1.5 \times 10^{-8} \Omega m$       C:  $\rho = 350 \times 10^{-8} \Omega m$

Magnitude of  $\rho$  determines whether the material is a conductor, an insulator, or a superconductor.


Colour coding:

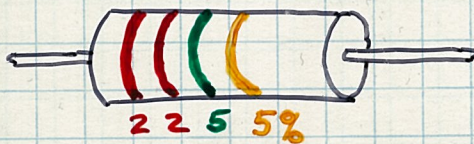


DH 1.7

$$\rightarrow 2200000 = 2.2 M\Omega \pm 5\%$$

Schematic representation:

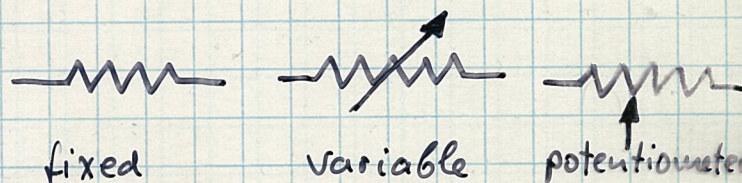

Note:  $R$  is never totally constant!

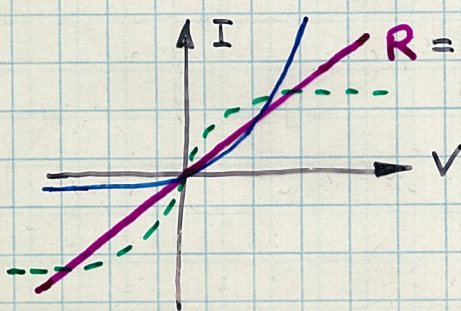

! Other V-I characteristics are possible

In general,  $R = R(V, I, t, \dots)$


**POWER**

$$P = IV = I^2R = \frac{V^2}{R}$$



$$1W = 1A \cdot 1V$$

Dissipation: heat, light, sound  
 Rate: size, surrounding medium


**SOURCES**

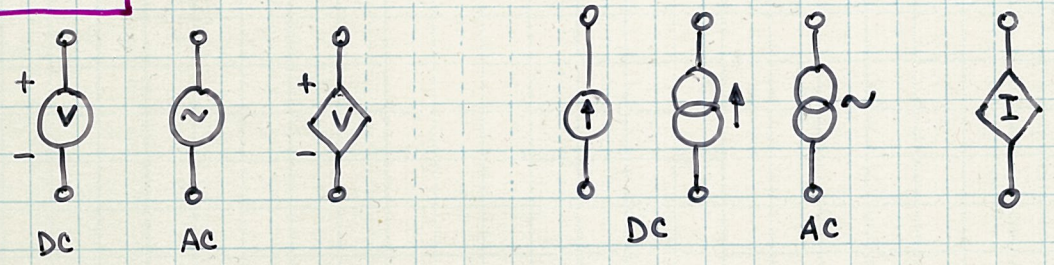

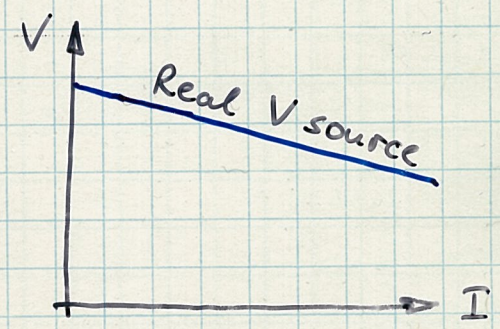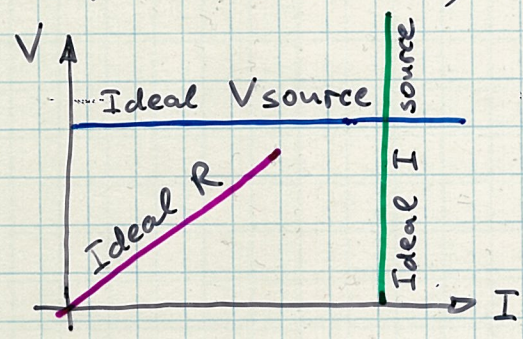
○ = independent (ideal)      ◇ = dependent (e.g. )



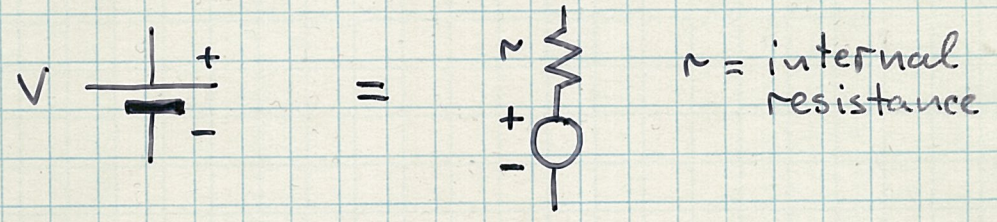
Representation of a dependent element via lumped parameter:



Adding sources:

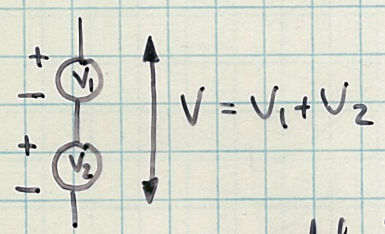


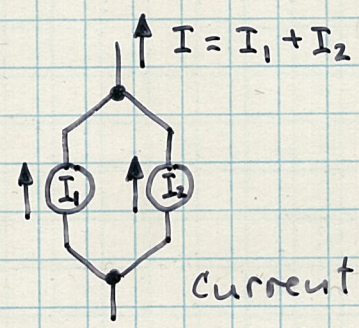Voltage sources add in series  
 Ideal voltage sources cannot be added in parallel, unless  $V_1 = V_2$




Current sources add in //  
 Ideal current sources cannot be added in series, unless  $I_1 = I_2$

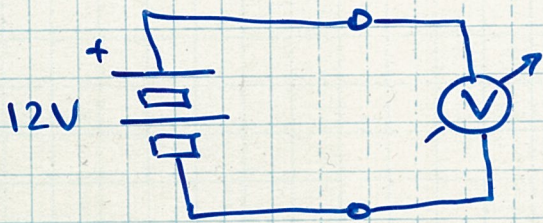70  
Ex What happens if an ideal 0-15V dc voltmeter is connected across a 12V car battery?




What happens if the voltmeter is replaced with an ammeter?

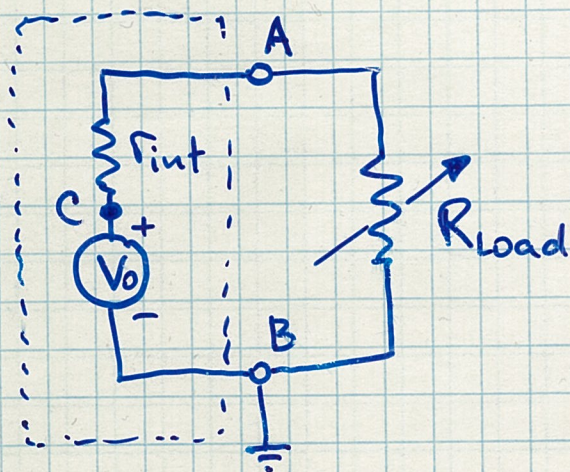Ex. Check if the following lumped circuit is adequate to model a real voltage source




# Water-flow analogy

Resistance :

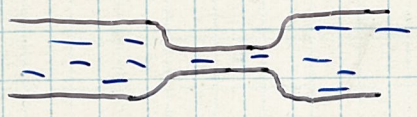


Ideal wires,  $R = \phi$   $\leftrightarrow$  large diameter pipes

Sources :

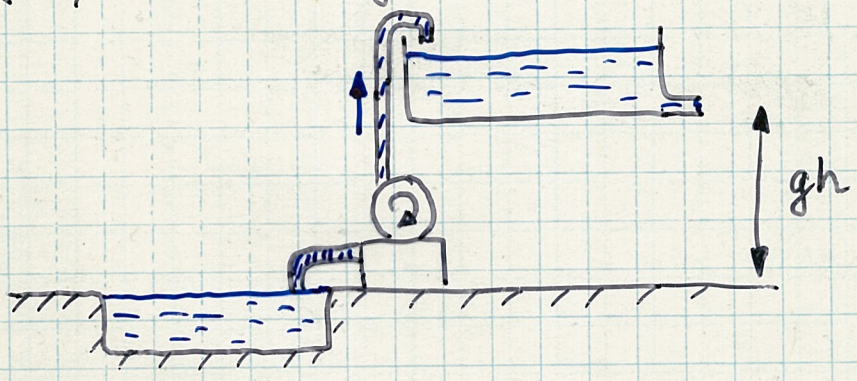
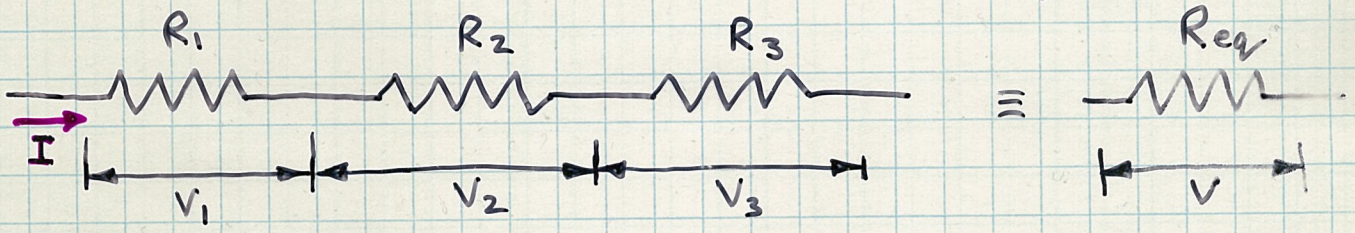
# Circuit reduction

Series : the current is the same in every component



$$\begin{aligned}
 V &= V_1 + V_2 + V_3 = \\
 &= IR_1 + IR_2 + IR_3 = \\
 &= I (R_1 + R_2 + R_3) \\
 &= I R_{eq}, \quad \text{where } R_{eq} = R_1 + R_2 + R_3
 \end{aligned}$$


$$R_{eq} = \sum_i R_i \quad \text{for a series circuit}$$

# Voltage divider

DH 1.9

$$V_1 = IR_1 = \frac{V}{R_{eq}} R_1 = \frac{R_1}{R_1 + R_2 + R_3} V$$

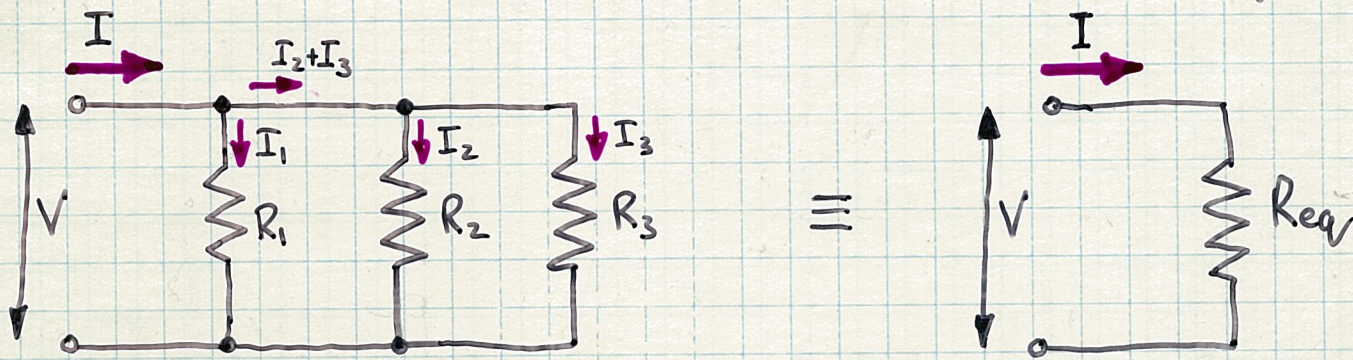Parallel: the voltage is the same across every component.



$$\begin{aligned}
 I &= I_1 + I_2 + I_3 = \\
 &= \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} = \\
 &= V \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) \\
 &= \frac{V}{R_{eq}}
 \end{aligned}$$

$$\frac{1}{R_{eq}} = \sum_i \frac{1}{R_i}$$

for a parallel circuit


Current divider

$$I_1 = \frac{V}{R_1} = \frac{I R_{eq}}{R_1} = I \frac{1/R_1}{1/R_{eq}} = I \frac{1/R_1}{1/R_1 + 1/R_2 + 1/R_3}$$

- current divides according to the inverse ratio of resistances.
- $1/R \equiv G$  conductance  $[G] = \frac{A}{V} = siemens = \Omega^{-1}$
- Complex circuits can be reduced by successive application of the above two rules.




Ex. Complex circuit reduction

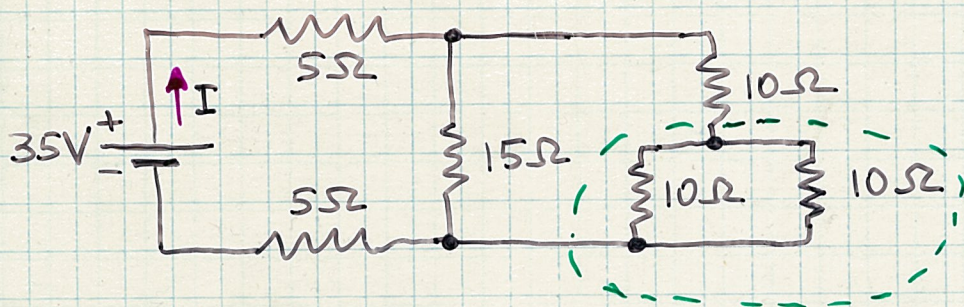


$$\frac{1}{R_{eq}} = \frac{1}{10} + \frac{1}{10} = \frac{2}{10}$$

$$R_{eq} = 5\Omega$$

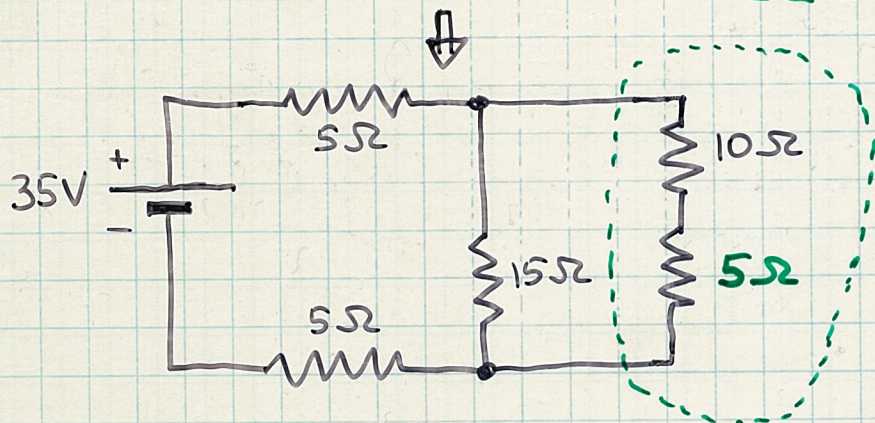


$$R_{eq} = 10 + 5 = 15\Omega$$

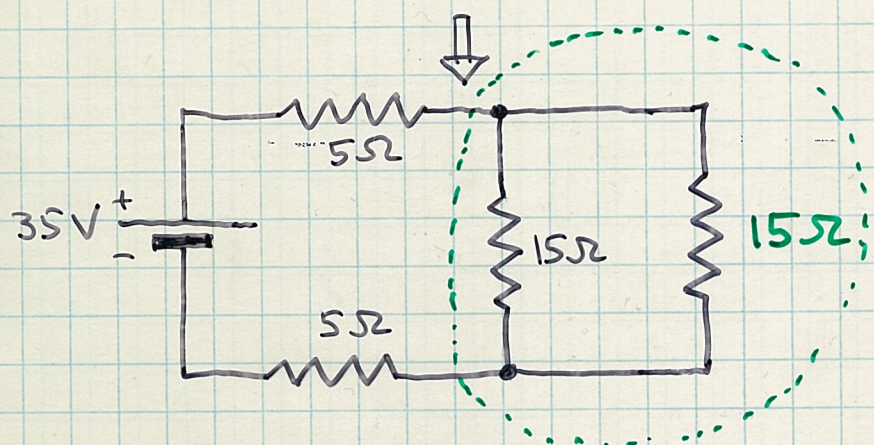


$$\frac{1}{R_{eq}} = \frac{1}{15} + \frac{1}{15} = \frac{2}{15}$$

$$R_{eq} = 7.5\Omega$$

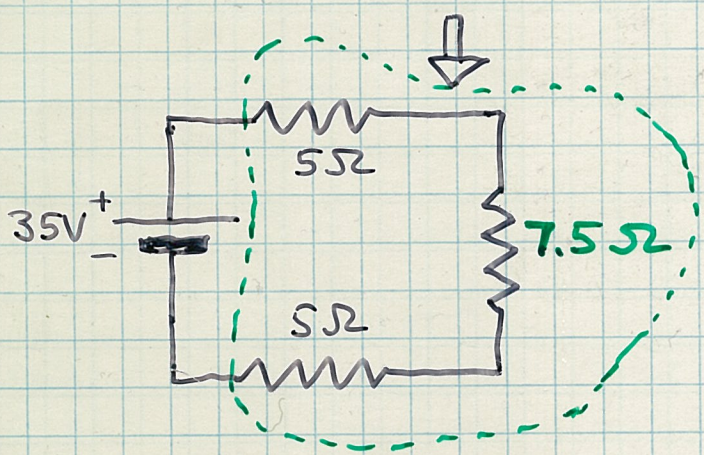


$$R_{eq} = 5 + 7.5 + 5 = 17.5\Omega$$

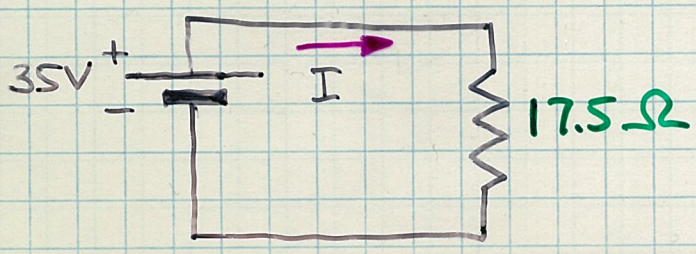

$$I = \frac{V}{R_{eq}} = \frac{35V}{17.5\Omega} = 2A$$
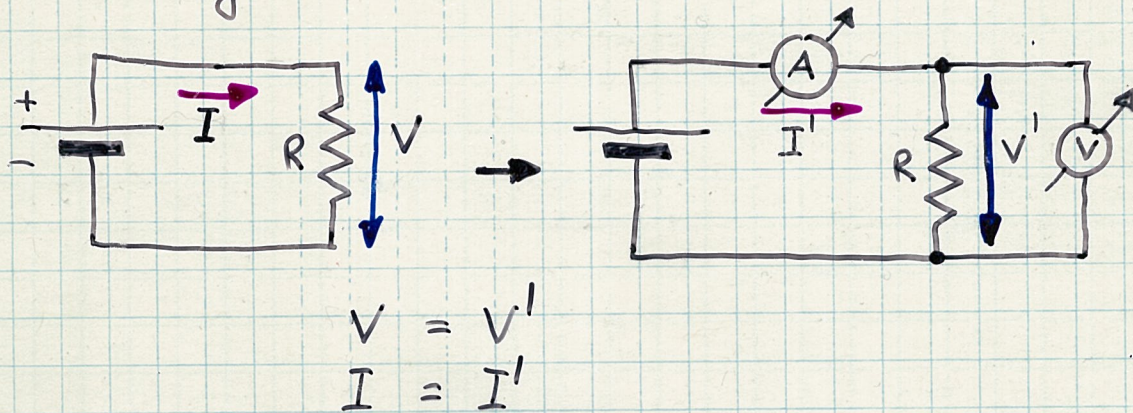
# Meters



- Ideal meters do not disturb the circuits they are measuring




$\Rightarrow$  ideal ammeter has no resistance,  $r_{int} = \emptyset$   
 ideal voltmeter has  $\infty$  resistance,  $r_{int} = \infty$

} consume NO power

- real meters

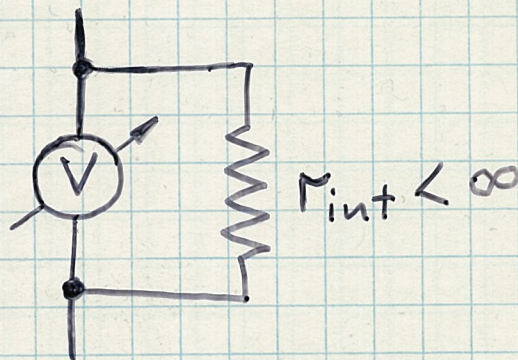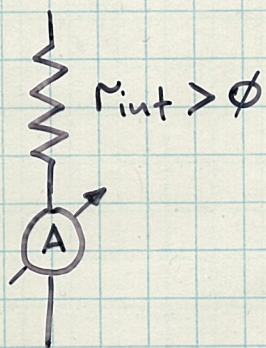

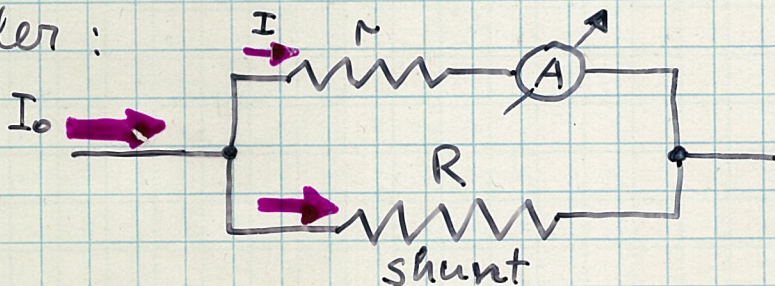
- measuring large currents: for large  $I$ , even a small resistance  $r_{int}$  will dissipate a lot of power,  $I^2 R$ .  $\Rightarrow$  need to use a current divider:



$$I = I_0 \frac{R}{R+r}$$

$R \ll r$

# Wheatstone bridge

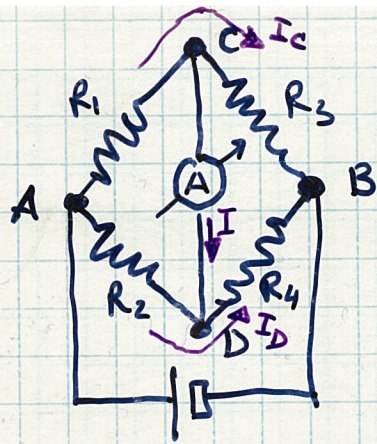

## Ex Null measurement


Adjust  $R_1, R_2, R_4$  until  $I = \phi$

Then:  $V_C = V_D$  or  $V_C - V_B = V_D - V_B$   
 $I_C R_3 = I_D R_4$

or  $V_A - V_C = V_A - V_D$   
 $I_C R_1 = I_D R_2$

$\Rightarrow \frac{R_1}{R_2} = \frac{R_3}{R_4}$  *unknown.*

## Ex.

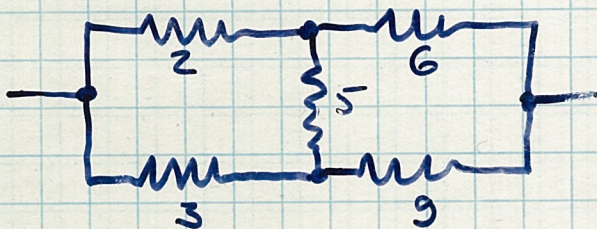

what is the current in the  $5\Omega$  resistor

## Ex Can we

