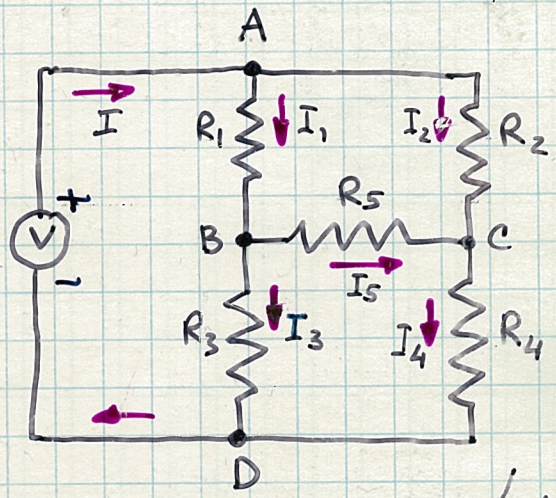


Kirchhoff's Laws

- Kirchhoff's Rules ; the underlying physical Laws are conservation of energy and charge.
- need KL for circuits that cannot be reduced by simple parallel/series pairing.
- will apply, but reduce to trivial cases in those circuits.

Wheatstone bridge :


! cannot be reduced!



NODE : ≥ 3 circuit elements connected



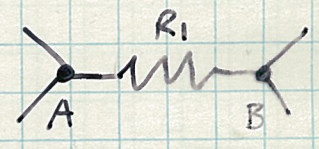BRANCH : an element that connects two adjacent nodes



LOOP : a path that begins at one node, passes one or more nodes, and ends at the node it started

ABDCA
ABCA


MESH : a loop containing no branches in its interior (= elementary loop)

ABCA
BCDB

- above : 4 nodes
- 6 branches
- 7 loops ; of these:
- 2 meshes

KCL

Σ currents flowing into a node is zero

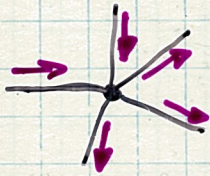


in: +ve
out: -ve

Σ I_i = 0

- expresses the conservation of charge
- water-flow analogy: no leaks (cons. of mass)

KVL

Σ voltage drops around a loop is zero

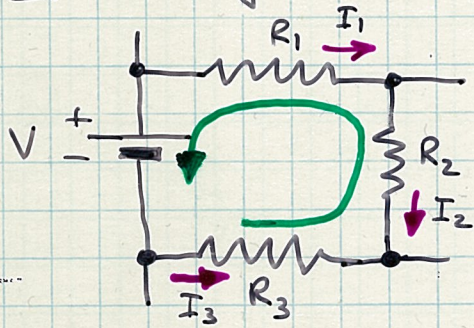

+I₁R₁ + I₂R₂ - I₃R₃ - V = 0

watch the signs!

- expresses the conservation of energy
- a form of the Ohm's Law; reproduces V=IR

Ex. The Wheatstone bridge circuit

- KCL → 4 equations, one for each node

A: I = I₁ + I₂ (1) B: I₁ = I₃ + I₅ (2) C: I₂ + I₅ = I₄ (3) D: I₃ + I₄ = I

Note: not independent, add the first 3 to get the 4th

- KVL → 3 independent equation, one for each mesh

I₁R₁ + I₃R₃ - V = 0 (4)
 I₁R₁ + I₅R₅ - I₂R₂ = 0 (5)
 I₃R₃ - I₄R₄ - I₅R₅ = 0 (6)


Note: other loops generate equations that can be obtained by combining these three; e.g.

ABCD: $I_1 R_1 + I_5 R_5 + I_4 R_4 - V = \phi$
is (4) - (6)

- # of unknowns = # of branches
 \Rightarrow 6 equations, 6 unknowns
- Always: # equations = (# nodes - 1) + (# meshes)

Getting the signs right

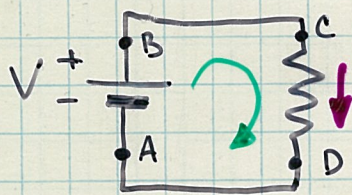- for a source, $V_+ > V_-$
- for a resistor, the current flows from higher to lower potential.



① start at A. $V_B > V_A \Rightarrow$ the source will contribute $+V$ as we go from A to B.

② $V_B = V_C \Rightarrow$ contribution = ϕ

③ $V_D < V_C \Rightarrow$ contribution is $-IR$

④ $V_D = V_A \Rightarrow$ contribution is $= \phi$

KVL: $\sum V_i = \phi$


$+V - IR = \phi$

• could have chosen to go around the loop in the opposite direction, against the current:

AD: ϕ DC: $+IR$ CB: ϕ BA: $-V \Rightarrow$ $+IR - V = \phi$

\Rightarrow identical result! $IR = V$, Ohm's Law.

"Wrong" current direction

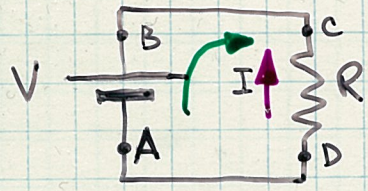


AB: +V
 BC: ϕ
 CD: +IR, since $V_C < V_D$ according to our choice of direction of I
 DA: ϕ

KVL: $\sum V_i = \phi = +V + IR \Rightarrow I = -\frac{V}{R}$

The minus sign means that the actual direction of I is opposite to the one chosen. !!

Ex.

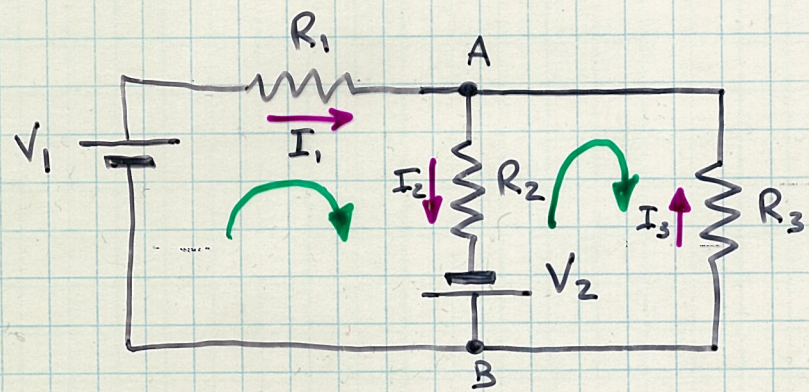

See also:
DH. Ex. 1.3

KCL @ A: $+I_1 - I_2 + I_3 = \phi$
 KCL @ B: $-I_1 + I_2 - I_3 = \phi$

} the same eq-n! (1)

KVL @ LHS loop: $+V_1 - I_1 R_1 - I_2 R_2 + V_2 = \phi$ (2)

KVL @ RHS loop: $-V_2 + I_2 R_2 + I_3 R_3 = \phi$ (3)

\Rightarrow 3 eq-us, 3 unknowns (I_1, I_2, I_3)


Note:
(2) + (3) yields
 $+V_1 - I_1 R_1 - \cancel{I_2 R_2} + \cancel{V_2} - \cancel{V_2} + \cancel{I_2 R_2} + I_3 R_3 = 0$
 $+V_1 - I_1 R_1 + I_3 R_3 = 0$ the big loop!

one current
] cf. the answer given in F.

The principle of SUPERPOSITION

A current in a branch of a linear circuit is equal to the sum of the currents produced by each source individually, i.e. with other sources set to zero.

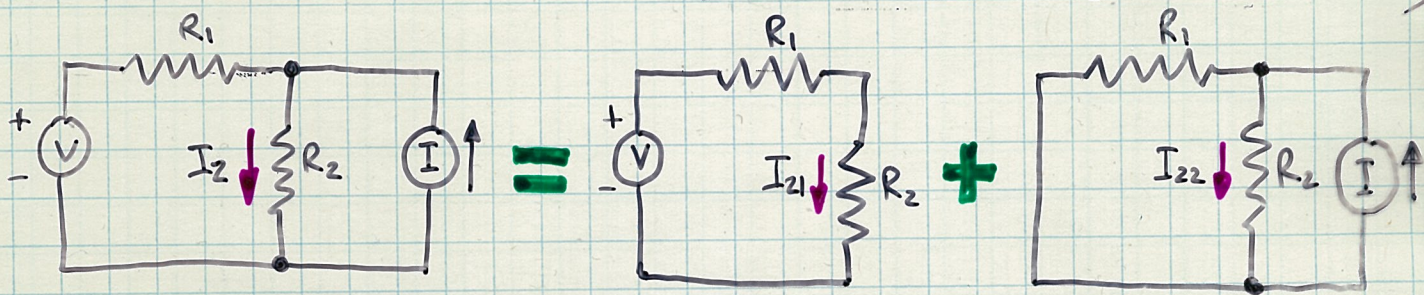- ideal sources, R (linear V - I -characteristics)
Kirchhoff's Laws \rightarrow linear equations
- setting sources to zero:
Voltage source \rightarrow short circuit (NO voltage)
current source \rightarrow open circuit (NO current)




$$I_2 = I_{21} + I_{22}$$

DH.L10

Loop current technique

Maxwell's method
Mesh equation method

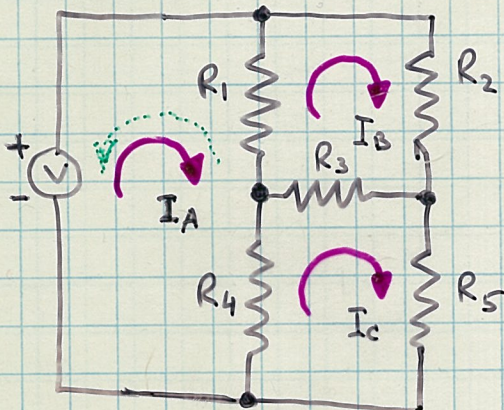

- closed loops: KCL is automatically satisfied (every loop current into a node also flows out of that node)
- apply KVL to each mesh
WATCH SIGNS!

Loop A: $(I_A - I_B)R_1 + (I_A - I_C)R_4 - V = \phi$

B: $(-I_A + I_B)R_1 + I_B R_2 + (I_B - I_C)R_3 = \phi$

C: $(-I_A + I_C)R_4 + (I_C - I_B)R_3 + I_C R_5 = \phi$

In matrix form :

$$\begin{pmatrix} R_1 + R_4 & -R_1 & -R_4 \\ -R_1 & R_1 + R_2 + R_3 & -R_3 \\ -R_4 & -R_3 & R_3 + R_4 + R_5 \end{pmatrix} \begin{pmatrix} I_A \\ I_B \\ I_C \end{pmatrix} = \begin{pmatrix} V \\ \phi \\ \phi \end{pmatrix}$$

General (vector) form of the Ohm's Law :

$$R \vec{I} = \vec{V} \Leftrightarrow \begin{pmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix}$$

with

• $R_{11} = \Sigma$ of all resistances in which mesh current I_A flows

$R_{12} = \Sigma$ ———— $I_A I_B$ flows

R_{12} is +ve if I_1, I_2 in the same direction
-ve if I_1, I_2 in the opposite directions.

$R_{13} = \Sigma$ ———— $I_A I_C$ flows


etc.

• Resistance matrix R is symmetric : $R_{ij} = R_{ji}$

• $V_i = \Sigma$ of all voltages driving I_i ;
 V_i is +ve if in direction of I_i , -ve if opposite

• unknowns : $\vec{I} = \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix}$ solve by matrix methods

Ex.

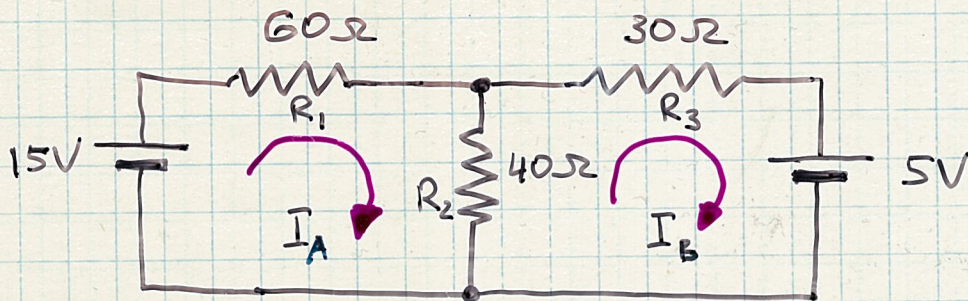

$$\text{Mesh A: } 15 = 60I_A + 40(I_A - I_B) = 100I_A - 40I_B \quad (1)$$

$$\text{B: } -5 = 30I_B + 40(I_B - I_A) = -40I_A + 70I_B \quad (2)$$

$$(1) \times 0.4 + (2): (40I_A - 16I_B) + (-40I_A + 70I_B) = 15 \times 0.4 - 5$$

$$\text{Through } R_3: 54I_B = 1 \Rightarrow \underline{I_B = 0.0185A}$$

$$\text{Through } R_1: 40I_A = 5 + 70I_B \Rightarrow \underline{I_A = 0.157A}$$

$$\text{Through } R_2: \underline{I_A - I_B = 0.139A}$$

- Note: $I_A - I_B > 0$ determines the true direction of the current in R_2 .

• "straight" KL method

- KCL: (# of nodes) - 1 eqs

KVL: (# of meshes) eqs.

- Directly obtain currents in each branch.

More equations,
straightforward answers

Mesh method

- (# of meshes) eq-s

- Obtain loop currents;
branch currents are
linear combinations

Fewer equations,
answers need some
interpreting