
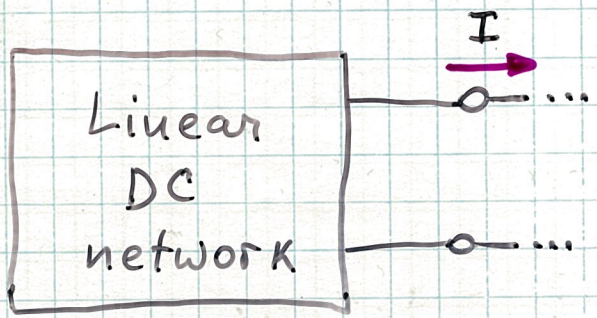


Equivalent Circuits

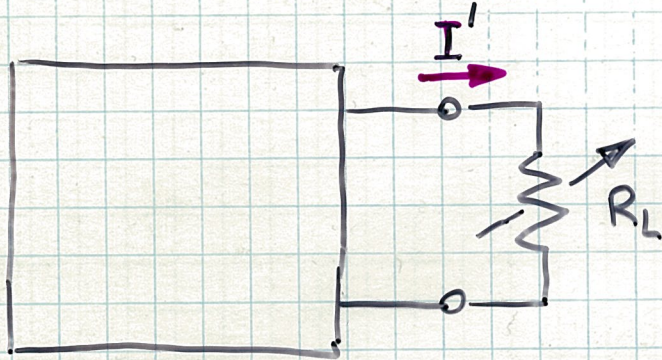


Consider a "black box" containing a combination of many linear elements (resistors, sources)



Connect to a load:
 Current I' is due to internal sources only
 As $R_L \rightarrow \emptyset$, $I' = +I_{sc}$

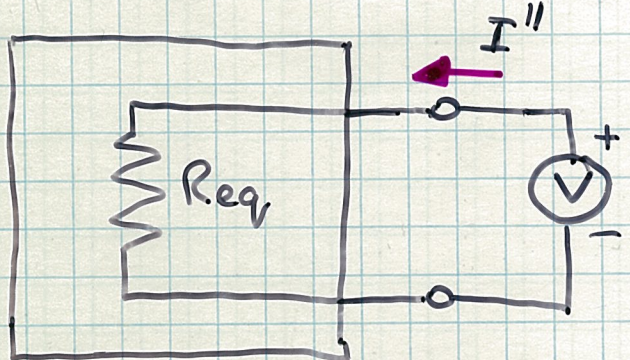Open up the box, turn off all the sources. What is left is a combination of R 's only \Rightarrow use our circuit reduction rules to find R_{eq}





Connect to a V source:
 Current I'' is due to external source(s) only


$$I'' = -\frac{V}{R_{eq}}$$

Turn internal sources back on. By principle of superposition:
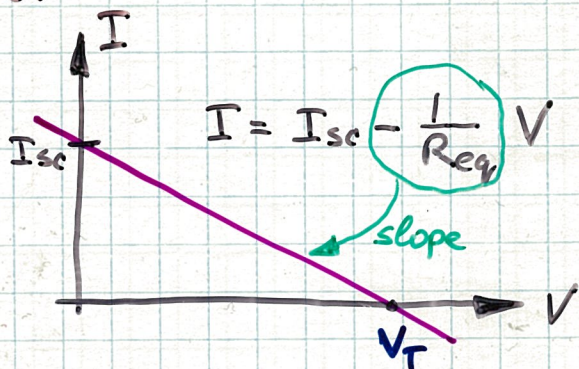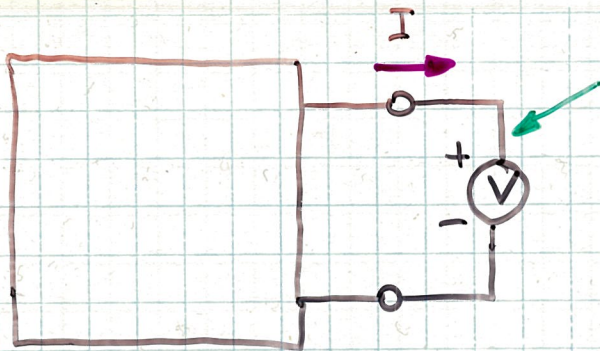
$$I = \underbrace{I_{sc}}_{\text{due to internal sources}} - \underbrace{\frac{V}{R_{eq}}}_{\text{due to external sources}}$$



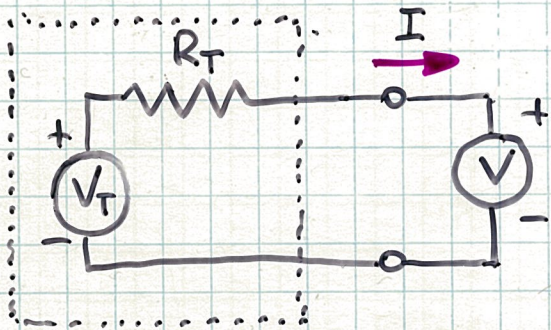Design a circuit that has exactly this V/I behaviour:



- $V = V_T \iff I = \emptyset$
- $V = \emptyset \iff I = \frac{V_T}{R_T}$
(short circuit)

Choose V_T, R_T so that : $\begin{cases} R_T = R_{eq} \leftarrow \text{from} \\ I = \frac{V_T}{R_T} = I_{sc} \leftarrow \text{before} \end{cases}$


If we now replace the "black box" (many components!) with the above $V_T + R_T$ circuit, there is no way to distinguish the two!

Thévenin's theorem

Any linear, two-terminal, DC network can be represented by a single voltage source in series with a resistor

In practice:


- open-circuit voltage, V_{oc} :

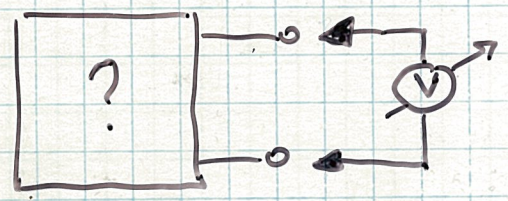

ideal voltmeter, $I \approx \phi$:

$$V_{oc} = V_T - IR_T \approx V_T$$

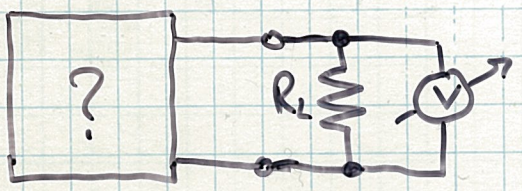- instead of short-circuit current, I_{sc} :





vary R_L until $V = \frac{1}{2} V_{oc}$:

$$\frac{1}{2} V_{oc} = IR_L = \frac{V_T}{R_T + R_L} R_L$$


$$\Rightarrow R_T + R_L = 2R_L \Rightarrow R_T = R_L$$

Another circuit is possible:

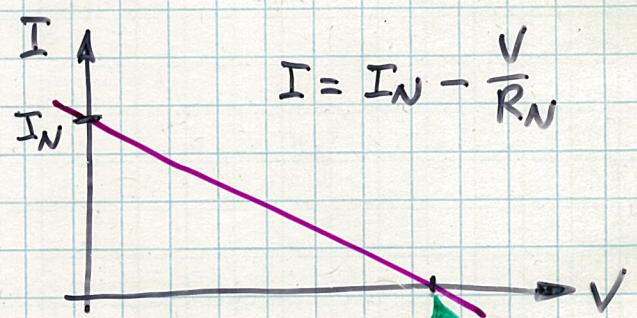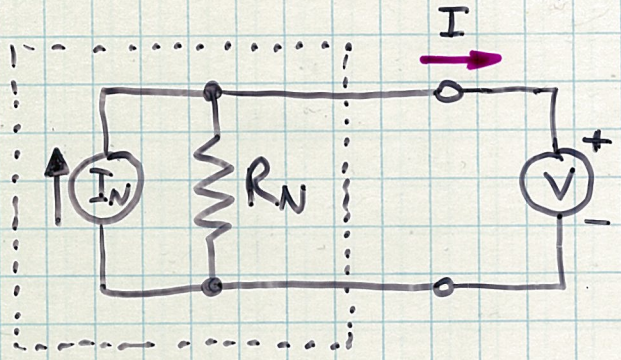

Use KCL: $I_N - I - \frac{V}{R_N} = \phi$

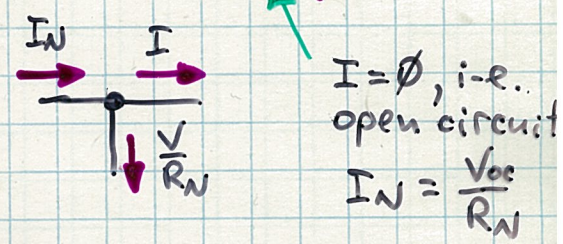Choose I_N, R_N :
$$\begin{cases} R_N = R_{eq} \\ I_N = \frac{V_{oc}}{R_N} \end{cases}$$



$I = \phi$, i.e. open circuit
 $I_N = \frac{V_{oc}}{R_N}$

Again, our $I_N + R_N$ circuit behaves exactly like the original "black box"

Norton's Theorem

Any linear, two-terminal, DC network can be represented by a single current source in parallel with a resistor.


The two theorems are obviously related!

EFTS : apply Norton's theorem to Thévenin's equivalent circuit



with : - Norton equivalent current, $I_N = I_{sc}$
 - Norton equivalent resistance, $R_N = V_{oc}/I_{sc} = R_T$

Ex. Voltage divider

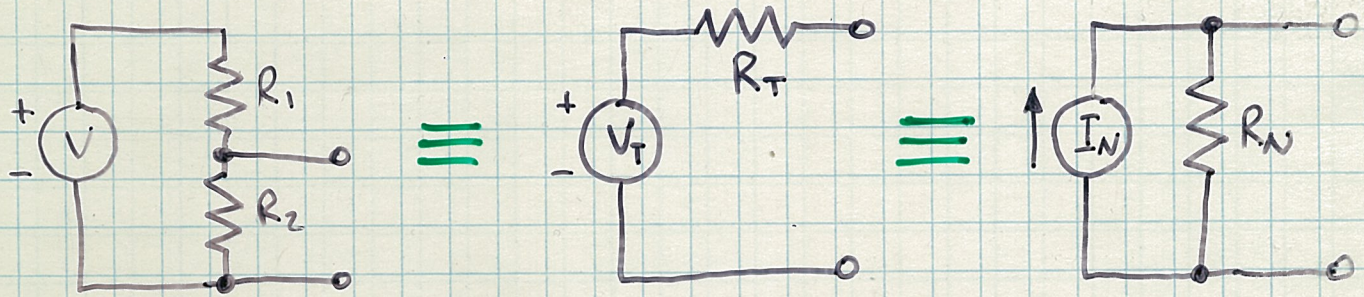

• oc voltage

$$V_T = V_{oc} = V \frac{R_2}{R_1 + R_2}$$

$$V_{oc} = I_N R_N$$

• sc current ($R_2 = \phi$)

$$I_{sc} = \frac{V}{R_1}$$

$$I_{sc} = I_N$$

\Rightarrow


$$R_T = V_T / I_{sc} = \frac{R_1 R_2}{R_1 + R_2} = R_N$$

! • power $P_{oc} = \frac{V^2}{R_1 + R_2}$

$$P_{oc} = \phi$$

$$P_{oc} = \frac{V^2 R_2}{R_1 (R_1 + R_2)}$$

Ex. Maximum power transfer

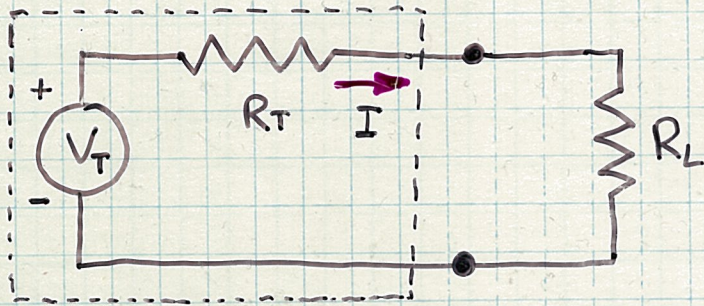

Power delivered to load \$R_L\$:

$$P = I^2 R_L = \left(\frac{V_T}{R_T + R_L} \right)^2 R_L$$

$$\Rightarrow P = \frac{V_T^2 / R_L}{(1 + R_T / R_L)^2}$$

\$\rightarrow \phi\$ as \$R_L \rightarrow \infty, R_L \gg R_T\$
 \$\rightarrow \phi\$ as \$R_L \rightarrow 0, R_L \ll R_T\$

Maximum in between:

$$\frac{dP}{dR_L} = \phi = \frac{V_T^2}{R_L} \frac{-2(-R_T/R_L^2)}{(1 + R_T/R_L)^3} + \frac{V_T^2}{(1 + R_T/R_L)^2} \frac{-1}{R_L^2}$$

$$\Rightarrow \phi = \frac{V_T^2}{R_L^2 (1 + R_T/R_L)^3} \left[\frac{2R_T}{R_L} - \left(1 + \frac{R_T}{R_L} \right) \right]$$

$$\Rightarrow 2 \frac{R_T}{R_L} = 1 + \frac{R_T}{R_L}$$

$$\Rightarrow \frac{R_T}{R_L} = 1$$

$$\boxed{R_L = R_T}$$

"Impedance matching" condition

- maximum power delivered to the load when the load resistance matches the internal resistance of the network.
- the best power transfer: $P = \frac{V_T^2}{4R_L} = P_{\text{internal}}$
- \$\Rightarrow\$ transfer efficiency \$\epsilon = 50\%\$