
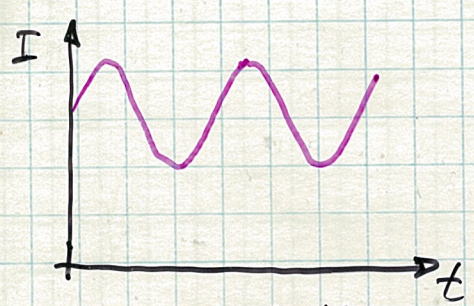



# Sinusoidal analysis

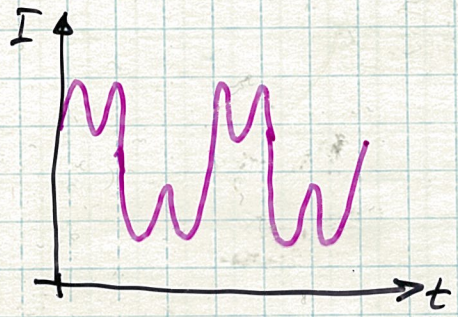


- sinusoidal time-dep.
- I always unidirectional
- ⇒ DC current + AC ripple



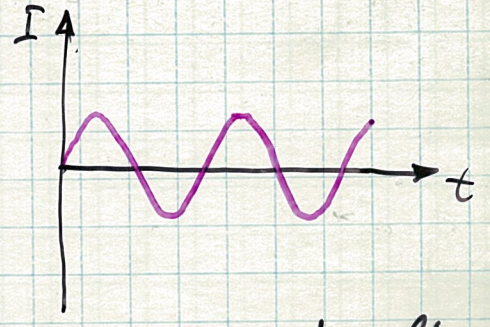
- non-sinusoidal, but periodic time dependence



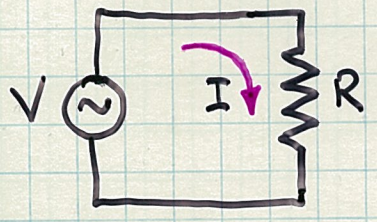- current alternating direction
- sinusoidal
- ⇒ AC + φ DC offset



$$V = V_0 \sin(\omega t + \phi)$$

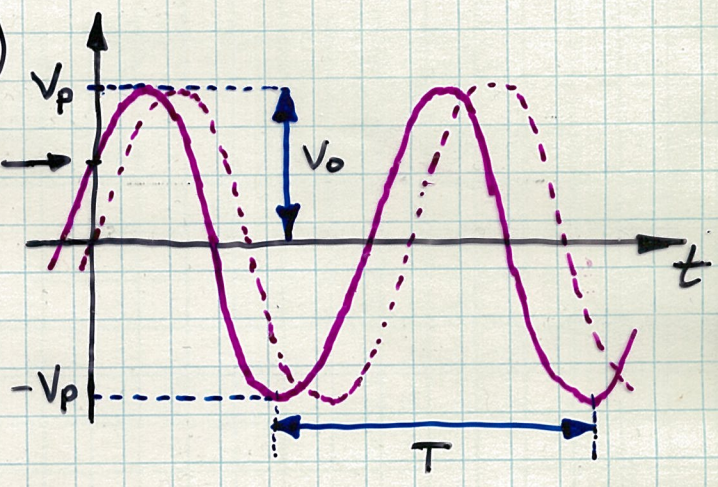

## Terminology

$T =$  period

$V_0 =$  amplitude

$V_{pp} =$  peak-to-peak voltage,  $V_p - (-V_p) = 2V_0$

$\omega =$  angular frequency (radians/s),  $\omega = 2\pi f = \frac{2\pi}{T}$

$f =$  frequency,  $\text{Hz} = \text{s}^{-1} = \frac{1}{T}$


$\phi =$  phase:  
 dotted line ↔ phase  $\phi = \phi$   
 solid line ↔ phase  $\phi > \phi$ , "ahead"

solid line leads the dotted line by  $\phi$   
 dotted line lags the solid line by  $\phi$  } equivalent
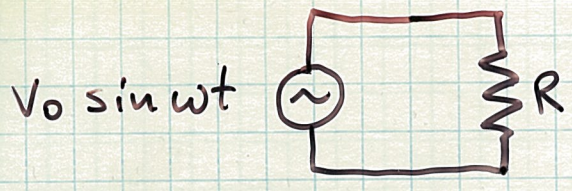
## Note

could have used  $\cos(\omega t + \phi) = \sin(\omega t + \phi')$   
 with  $\phi = \phi' + \frac{\pi}{2}$   
 ⇒ a difference of a phase factor.





$$I = \frac{V_0}{R} \sin \omega t$$

- Average power over one period :

$$\bar{P} = \frac{1}{T} \int_0^T I^2 R dt = \frac{1}{T} \int_0^T \frac{V_0^2}{R} \sin^2 \omega t dt = \frac{V_0^2}{2R}$$

⇒ another way of characterizing the voltage :

$$V_{rms} = \left[ \frac{1}{T} \int_0^T V^2(t) dt \right]^{1/2} = \frac{V_0}{\sqrt{2}} \approx 0.707 V_0$$

Useful because

$$\bar{P} = \frac{V_{rms}^2}{R}$$

Ex. "110V AC" →  $V(t) = (110 \times \sqrt{2}) \cos \omega t$


Aside

- representation by complex numbers

Euler's formula

$$e^{j\theta} = \cos \theta + j \sin \theta$$

$$j \equiv \sqrt{-1}$$

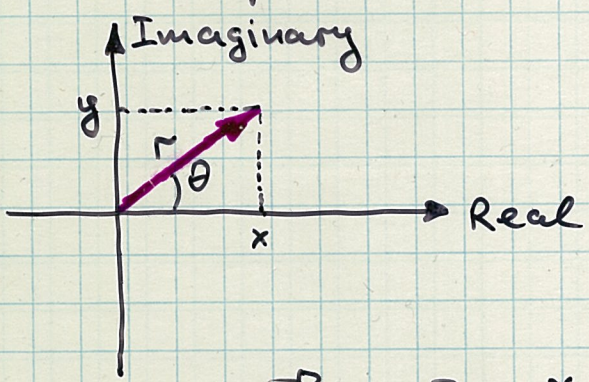

$$\begin{cases} x = r \cos \theta \\ y = r \sin \theta \end{cases}$$

$$\Rightarrow z = x + jy = r(\cos \theta + j \sin \theta) = r e^{j\theta}$$

$$\sin \theta = \text{Im}(z) = \frac{e^{j\theta} - e^{-j\theta}}{2j}$$

$$\cos \theta = \text{Re}(z) = \frac{e^{j\theta} + e^{-j\theta}}{2}$$




# Operations on complex numbers

## conjugation

$$z^* = x - jy$$

$$z^* = r e^{-j\theta}$$

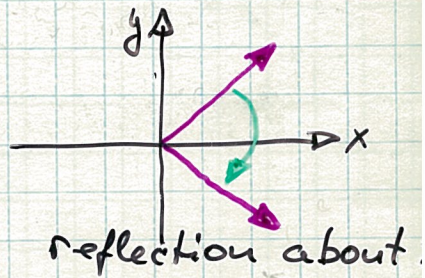

## addition

$$z_1 = x_1 + jy_1 \quad z_2 = x_2 + jy_2$$

$$z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$$

vector addition

## multiplication

$$z_1 z_2 = (x_1 + jy_1)(x_2 + jy_2) =$$

$$= x_1 x_2 + jy_1 x_2 + x_1 jy_2 + j^2 y_1 y_2$$

$$= (x_1 x_2 - y_1 y_2) + j(x_1 y_2 + x_2 y_1)$$

$$z_1 z_2 = (r_1 e^{j\theta_1})(r_2 e^{j\theta_2}) = r_1 r_2 e^{j(\theta_1 + \theta_2)}$$


## division

$$\frac{z_1}{z_2} = \frac{x_1 + jy_1}{x_2 + jy_2} = \frac{(x_1 + jy_1)(x_2 - jy_2)}{(x_2 + jy_2)(x_2 - jy_2)}$$

$$= \frac{x_1 x_2 + y_1 y_2}{x_2^2 + y_2^2} + j \frac{y_1 x_2 - x_1 y_2}{x_2^2 + y_2^2}$$

$$\frac{z_1}{z_2} = \frac{r_1 e^{j\theta_1}}{r_2 e^{j\theta_2}} = \frac{r_1}{r_2} e^{j(\theta_1 - \theta_2)}$$

## useful relations

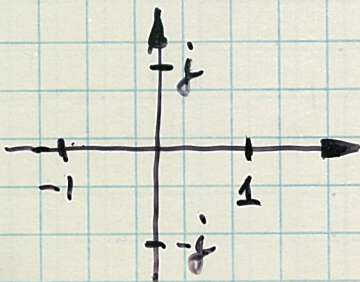

$$|z|^2 = z z^* = x^2 + y^2 = r^2$$

$$j^2 = -1 \Rightarrow \frac{1}{j} = \frac{j}{j^2} = \frac{j}{-1} = -j$$

$$j = \cos \frac{\pi}{2} + j \sin \frac{\pi}{2} = e^{j\pi/2}$$

$$-j = \frac{1}{j} = e^{-j\pi/2}$$




# Phasor notation: equivalent to exponential

write  $z = r e^{j\theta}$  as  $z = r \angle \theta$


For example,  $z_1 z_2 = r_1 r_2 e^{j(\theta_1 + \theta_2)} = (r_1 r_2) \angle (\theta_1 + \theta_2)$

## Resistance

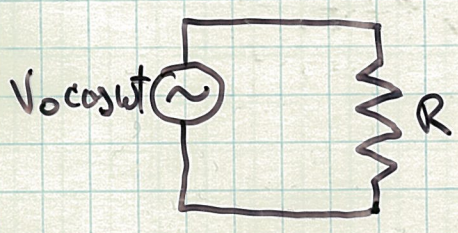


$$V(t) = V_0 \cos \omega t = \text{Re} [ V_0 e^{j\omega t} ]$$

$$I_R(t) = \frac{V_0}{R} \cos \omega t$$

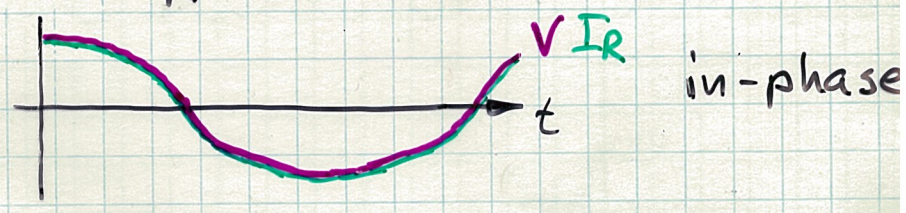


in-phase

## Capacitance

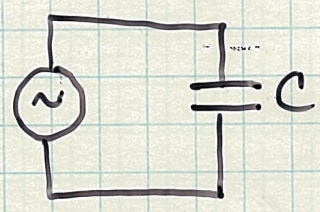

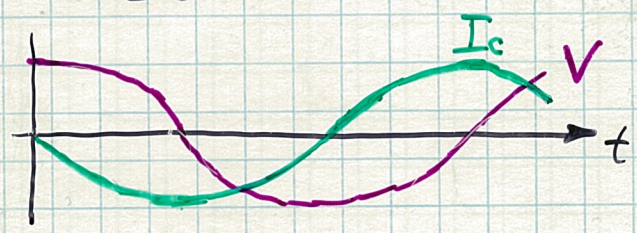
$$I_c = C \frac{dV}{dt} = -\omega C V_0 \sin \omega t$$
$$= \text{Re} [ j\omega C V_0 e^{j\omega t} ]$$




$\Delta\phi = \frac{\pi}{2}$   
I leads V

## Inductance

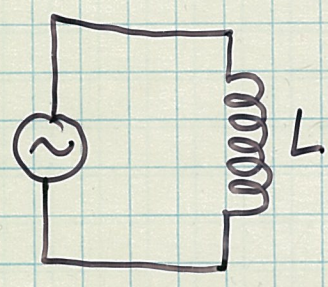
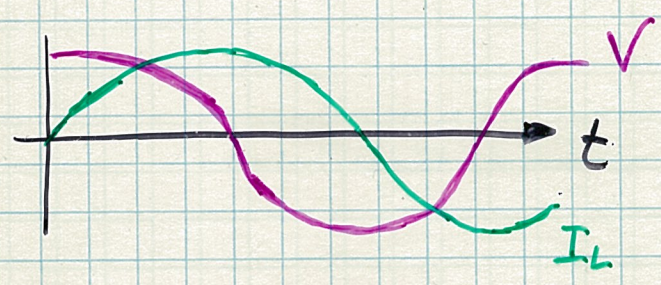
$$I_L = \frac{1}{L} \int V dt = \frac{V_0}{\omega L} \sin \omega t$$



$\Delta\phi = -\frac{\pi}{2}$   
I lags V




## Summary

$$V = V_0 e^{j\omega t}$$

$$I_R = \frac{V_0}{R} e^{j\omega t}$$

$$I_C = j\omega C V_0 e^{j\omega t} = \omega C V_0 e^{j(\omega t + \pi/2)}$$
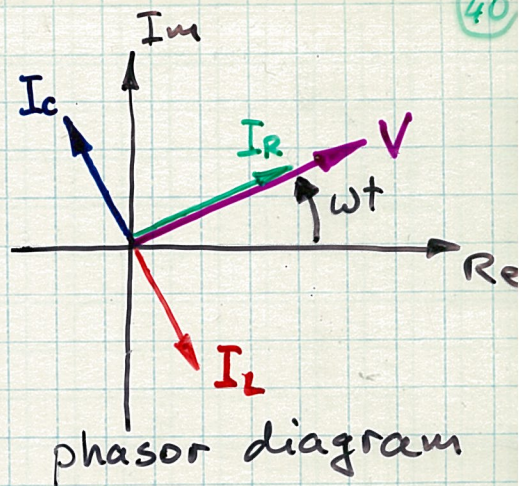
$$I_L = \frac{V_0}{j\omega L} e^{j\omega t} = \frac{V_0}{\omega L} e^{j(\omega t - \pi/2)}$$



$I_C$  leads  $V$  by  $90^\circ$

$I_L$  lags  $V$  by  $90^\circ$

Only  $I_R$  is in-phase with  $V$

This is the so-called frequency-domain representation

In frequency domain, the ratio of  $V$  to  $I$  is time-independent!  $\Rightarrow$  generalize to the complex form of Ohm's Law:

$$V = IZ$$

AC Ohm's Law

$Z \equiv$  impedance

$$Z_R = R$$

$$Z_C = \frac{1}{j\omega C}$$

$$Z_L = j\omega L$$

$$= \frac{V}{I} \text{ (generalized)}$$



$\Rightarrow$  complex algebraic equations replace differential equations needed for time-domain solutions

$\Rightarrow$  solutions are complex, with amplitude and phase

$\Rightarrow$  impedance is a purely sinusoidal concept, not good for transients



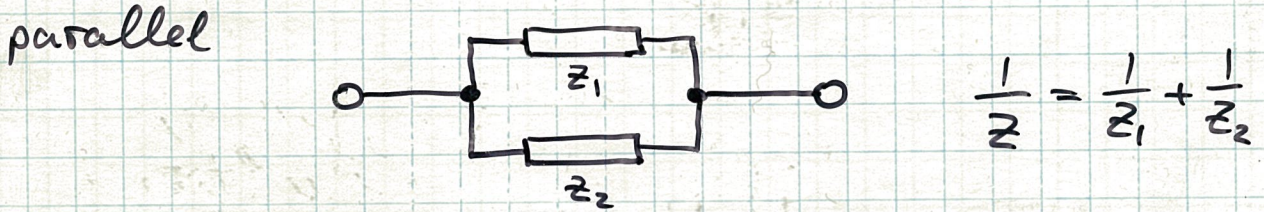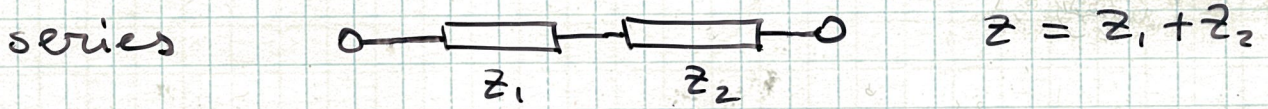- using impedance, can treat all components as "resistors":



- magnitude of impedance is called reactance

$$X_R = R \quad X_C = \frac{1}{\omega C} \quad X_L = \omega L$$


reciprocal of impedance is called admittance

→ angle to x-axis is equal & opposite to that of impedance.

- arbitrary circuit element



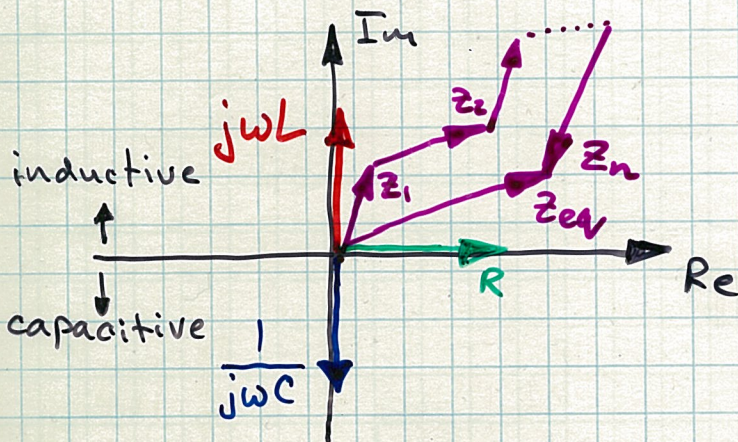vector (not a phasor!)  
 $e^{j\omega t}$  factors out of  $\frac{V}{I}$



$$Z_C = \frac{1}{j\omega C} \propto \frac{1}{j} = -j$$

$$Z_L = j\omega L \propto j$$

$$Z_{eq} = Z_1 + Z_2 + \dots + Z_n$$

(series connection)

- average power

$$\bar{P} = \frac{1}{T} \int_0^T V I dt$$


$$- V_C \sim \cos \omega t \Rightarrow I_C = C \frac{dV}{dt} \sim -\sin \omega t \Rightarrow \bar{P} \sim \int_0^T \sin \omega t \cos \omega t dt = 0$$

$$- V_L \sim \cos \omega t \Rightarrow I_L = \frac{1}{L} \int V dt \sim \sin \omega t \Rightarrow \bar{P} = 0$$

→ no energy dissipation - E stored for release 1/2 cycle later



## Time-domain solution

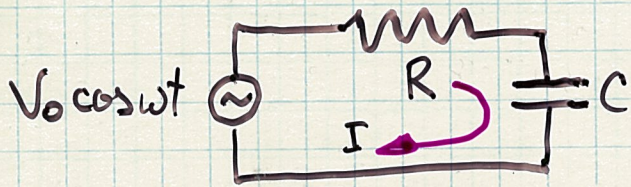

KVL:  $V_0 \cos \omega t = IR + \frac{1}{C} \int I dt$

$$\Rightarrow \frac{dI}{dt} + \frac{1}{RC} I = -\frac{\omega V_0}{R} \sin \omega t$$

1st order, non-homogeneous, the RHS is time-dependent D.E.

### Highlights:

1. Guess a general sol-n

$$I = I_1 \sin \omega t + I_2 \cos \omega t$$

2. substitute and solve for sin and cos terms separately:

$$I_1 = -\frac{\omega C V_0}{\omega^2 R^2 C^2 + 1}$$

$$I_2 = \frac{\omega^2 R C^2 V_0}{\omega^2 R^2 C^2 + 1}$$

3. combine as

$$I = \frac{\omega C V_0}{\omega^2 R^2 C^2 + 1} (\omega R C \cos \omega t - \sin \omega t)$$

or


$$I = \frac{V_0}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} \cos(\omega t + \varphi)$$

with  $\varphi = \arctan\left(\frac{1}{\omega R C}\right)$  ↔

4.  $V_R = IR = \dots$

$$V_C = \frac{1}{C} \int I dt = \dots$$

## Frequency-domain solution (42)

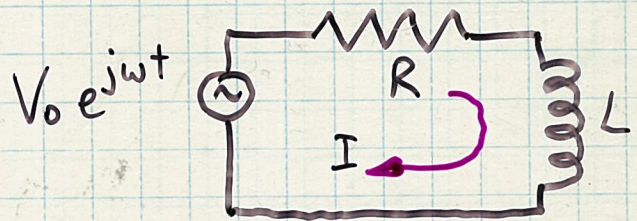

$$Z_{L+R} = R + j\omega L$$

$$I = \frac{V_0}{R + j\omega L} e^{j\omega t}$$

I<sub>0</sub>

Algebraic eq-n


$$I_0 = \frac{V_0 (R - j\omega L)}{(R + j\omega L)(R - j\omega L)} = \frac{V_0 (R - j\omega L)}{R^2 + \omega^2 L^2}$$

To find phase:

$$x + jy = \sqrt{x^2 + y^2} e^{j\varphi}, \varphi = \arctan \frac{y}{x}$$

$$\Rightarrow I_0 = \frac{V_0}{\sqrt{R^2 + \omega^2 L^2}} e^{j\varphi}$$

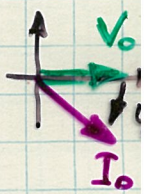with  $\varphi = \arctan \frac{-\omega L}{R}$



Finally:

$$I = \frac{V_0}{\sqrt{R^2 + \omega^2 L^2}} e^{j(\omega t + \varphi)}$$

Transform back to time domain:

$$e^{j(\omega t + \varphi)} \rightarrow \cos(\omega t + \varphi)$$

$$\Rightarrow I = \frac{V_0}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \varphi)$$


cf. with  $\varphi = \arctan \frac{-\omega L}{R}$



- Note 1. in RL circuit, the current lags voltage by amount intermediate between that for R ( $0^\circ$ ) and pure L ( $-90^\circ$ )

Similarly for RC: between R ( $0^\circ$ ) and pure C ( $+90^\circ$ )

- Note 2 operations on complex numbers:

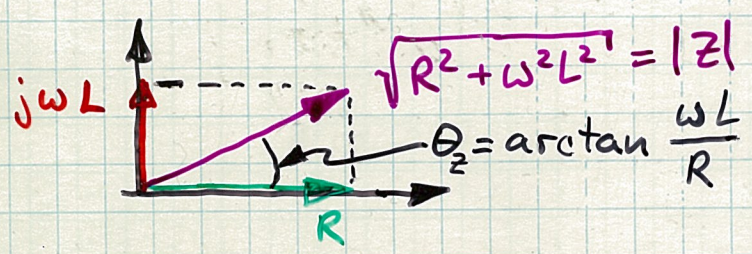

$$I_o \angle \theta_I = \frac{V_o \angle \theta_V}{Z_o \angle \theta_Z} = \frac{V_o}{Z_o} \angle \theta_V - \theta_Z$$

Here:  $\theta_V = \omega t$ ,  $\theta_Z = -\varphi$   
 $\Rightarrow \theta_I = \omega t + \varphi$


- Note 3 Electrical engineers' struggle for "cosφ"

$$\begin{aligned} \text{Power factor} &= \frac{\text{Power dissipated by } Z}{\text{Apparent power} = V_{\text{rms}} I_{\text{rms}}} \\ &= \frac{\text{Re}(Z)}{|Z|} = \cos \varphi \\ |Z| &= [(Re Z)^2 + (Im Z)^2]^{1/2} \end{aligned}$$

! no power dissipation in pure C or L

For example, add C to inductive loads (motors) to reduce  $Im Z$ .

- Ex.

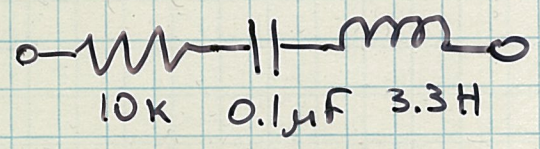

$$Z_R = R = 10 \times 10^3 = 10^4$$

$$\begin{aligned} Z_C &= -j \frac{1}{\omega C} = -j \frac{1}{2\pi \times 440 \times 0.1 \times 10^{-6}} \\ &= -j 3617 \end{aligned}$$

$$\begin{aligned} Z &= Z_R + Z_C + Z_L = \dots \\ &= 10,000 + j 5506 \Omega \end{aligned}$$

$$Z_L = j\omega L = j 2\pi \times 440 \times 3.3 = j 912$$