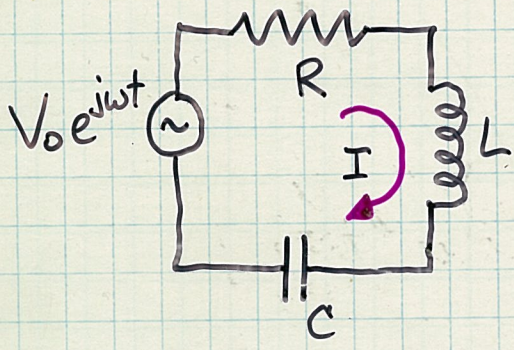


RESONANCE

Series RCL circuit



$$Z = R + j\omega L + \frac{1}{j\omega C}$$

$$I = \frac{V_0 e^{j\omega t}}{Z} = I_0 e^{j\omega t}$$

$$I_0 = \frac{V_0}{Z} = \frac{V_0}{R + j(\omega L - 1/\omega C)}$$

$$\Rightarrow I_0 = \frac{[R - j(\omega L - 1/\omega C)] V_0}{R^2 + (\omega L - 1/\omega C)^2} = \frac{V_0}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}} e^{j\phi}$$

where $\phi = \arctan\left(\frac{1/\omega C - \omega L}{R}\right)$

* EFTS

→ Re-write in time domain:

$$I(t) = \frac{V_0}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}} \cos(\omega t + \phi)$$

Magnitude of phasor current $|I_0| = \max$, if


$$\omega = \omega_0 = \frac{1}{\sqrt{LC}}$$

$\omega_0 \equiv$ resonant frequency

At $\omega = \omega_0$: $\phi = 0$, $I_0 = \frac{V_0}{R} \Rightarrow$ purely resistive circuit

$\omega < \omega_0$: circuit looks capacitive

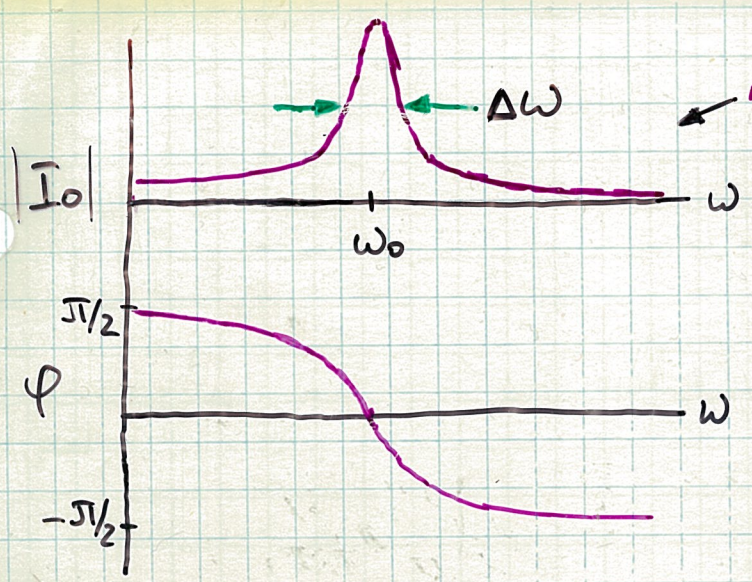$\omega > \omega_0$: circuit looks inductive



At resonance :

$$\omega = \omega_0 = (LC)^{-1/2}$$

$$\phi = \phi$$

$$Z = R$$

$$I_0 = \frac{V_0}{R}$$

$\Delta\omega$ = difference between half-power points, i.e.
 where $I = \frac{I_{max}}{\sqrt{2}} \Leftrightarrow \boxed{\omega L - \frac{1}{\omega C} = \pm R} (*)$

Rewrite (*) and solve:

$$\omega^2 \mp \frac{R}{L} \omega - \frac{1}{LC} = 0 \Rightarrow \begin{cases} \omega_h = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \\ \omega_e = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \end{cases}$$

$$\Rightarrow \Delta\omega = \omega_h - \omega_e = \frac{R}{L}$$


Quality factor of a circuit

$$Q \equiv \frac{\omega_0}{\Delta\omega} = \frac{\omega_0 L}{R}$$


• Note: $Q = \frac{X_L}{R} = \frac{X_C}{R}$ since on resonance:

$$X_L \equiv \omega L \Big|_{\omega=\omega_0} = \omega_0 L \quad \text{and} \quad X_C \equiv \frac{1}{\omega C} \Big|_{\omega=\omega_0} = \frac{\omega_0}{\omega_0^2 C} = \frac{\omega_0}{\frac{1}{LC}} = \omega_0 L$$

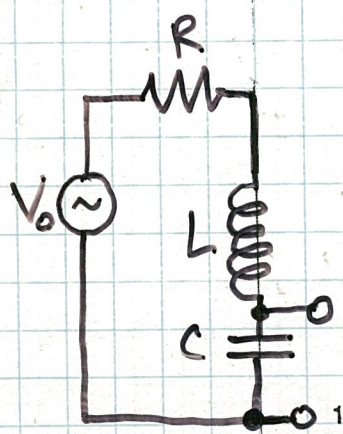
• Note: C & L determine ω_0 (frequency)
 R & L determine $\Delta\omega$ (width, i.e. the time constant)



$$\text{Gain} = \frac{V_C}{V_0}$$

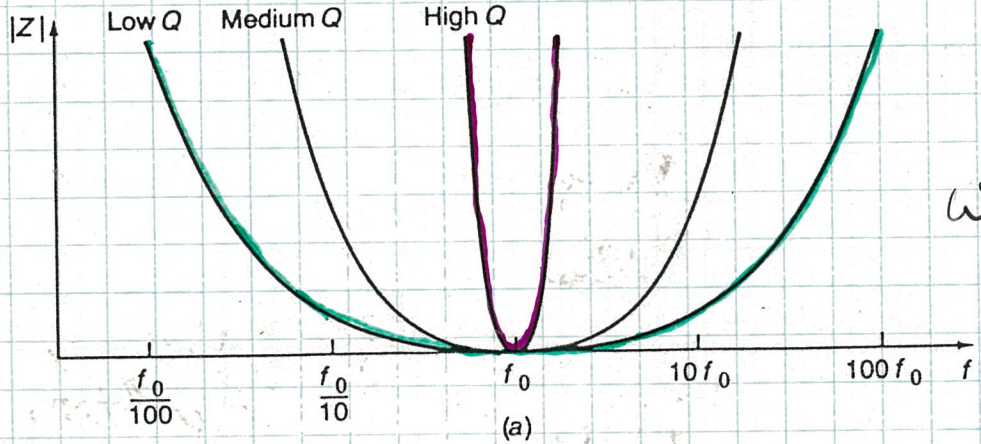
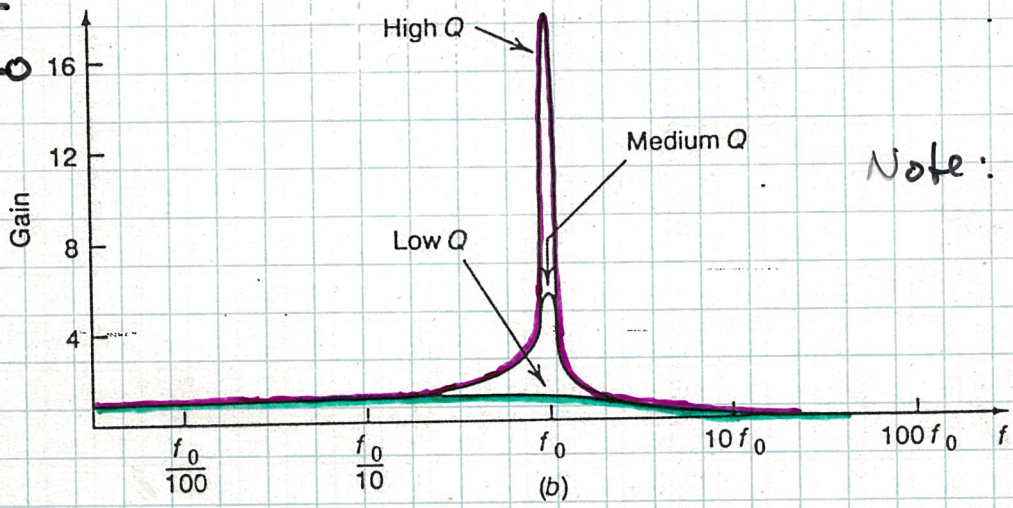
$$\omega_0 = 2\pi f_0 = \frac{1}{\sqrt{LC}}$$



Note: not symmetric

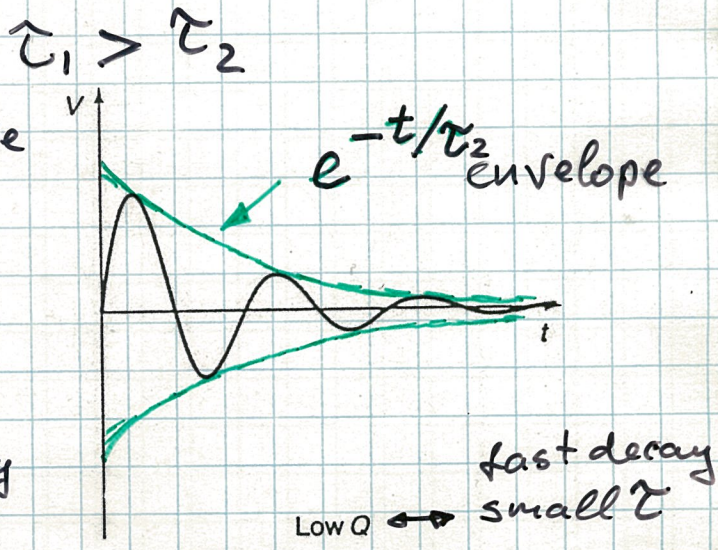
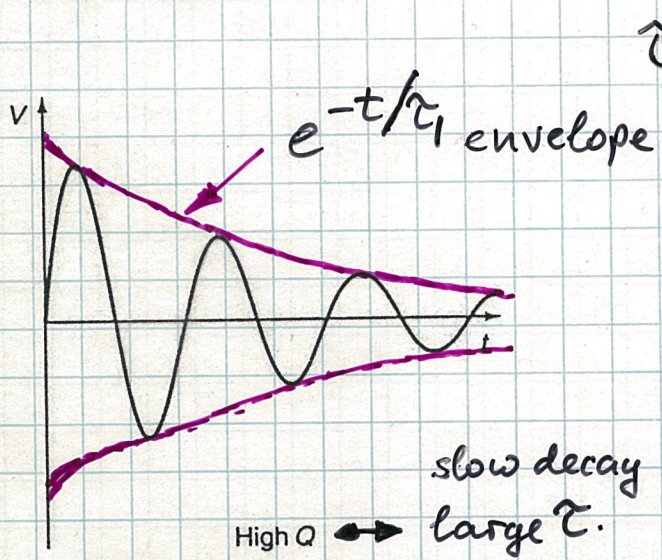


FIGURE 10-3 The effect of Q on the lifetime of a decaying oscillation.

Recall:

$$\alpha_{1,2} = -\frac{R}{2L} \pm \dots \Rightarrow \tau \sim \frac{L}{R} \sim \frac{1}{\Delta\omega}$$

- Calculate voltages across components on-resonance:

$$V_R = IR = V_0 \cos \omega_0 t \quad \equiv \text{source voltage}$$

$$\left. \begin{aligned} V_C &= \frac{1}{C} \int I dt = \frac{\omega_0 L}{R} V_0 \sin \omega_0 t \\ V_L &= L \frac{dI}{dt} = -\frac{\omega_0 L}{R} V_0 \sin \omega_0 t \end{aligned} \right\} \begin{array}{l} \text{Equal, opposite,} \\ \text{and } 90^\circ \text{ out-of-} \\ \text{phase with source} \end{array}$$

NB: $|V_L|, |V_C| = Q V_0 \leftarrow \text{can be } \gg V_0!$
 resonant high-Q circuit \rightarrow HIGH VOLTAGES!

Ex.1. radio antenna circuit.


High Q = high frequency selectivity
 = high sensitivity (gain)

Ex.2. speaker system.

Avoid resonances to provide broad frequency coverage \rightarrow Low Q

- Another definition for Q:
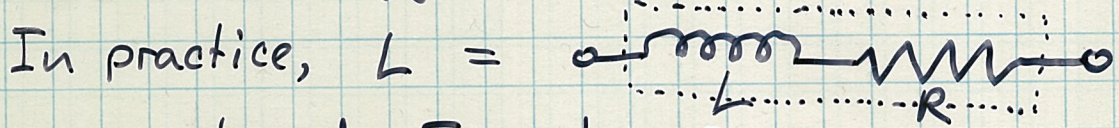
$$Q = \frac{\text{max energy stored}}{\text{energy dissipated per radian}}$$



- max stored $E = \frac{1}{2} L I_{\max}^2$

- E dissipated / radian = $\frac{I_{\text{av}}^2 R}{\omega} = \frac{I_{\max}^2 R}{2\omega}$

$\Rightarrow Q = \frac{\omega L}{R}$, as before.