
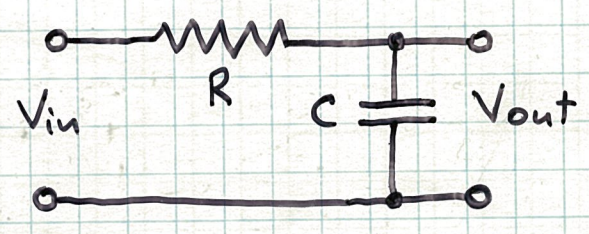


# Filter circuits

Filter: pass certain frequencies, reject others

## Low-pass filters

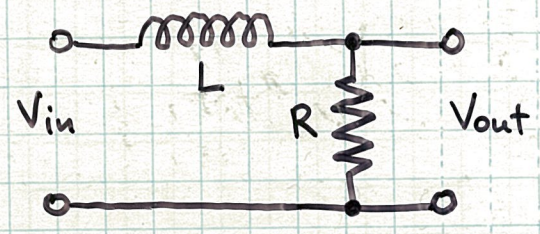

Examples of AC voltage dividers:

• RL case:  $V_{out} = \frac{R}{R + j\omega L} V_{in} = \frac{R^2 - j\omega RL}{R^2 + \omega^2 L^2} V_{in}$


$\Rightarrow \left| \frac{V_{out}}{V_{in}} \right| = \frac{R}{\sqrt{R^2 + \omega^2 L^2}} = \frac{1}{\sqrt{1 + (\frac{\omega L}{R})^2}} = \frac{1}{\sqrt{1 + (\omega/\omega_c)^2}}$

where  $\omega_c \equiv \frac{R}{L}$

Low  $\omega$ ,  $\omega \ll \omega_c \Rightarrow$  no attenuation,  $V_{out} = V_{in}$

High  $\omega$ ,  $\omega \gg \omega_c \Rightarrow V_{out} \rightarrow \emptyset$  **LOW-PASS**

$\omega = \omega_c$ ,  $\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{2}}$  ← half-power point

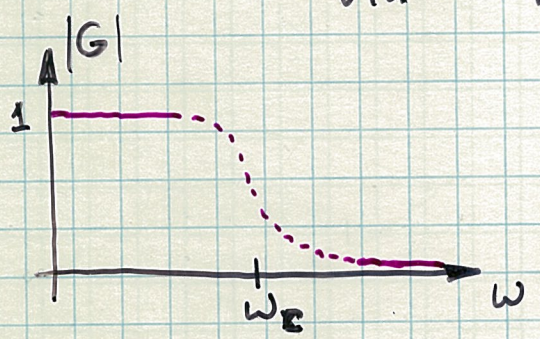

$\omega_c =$  angular cutoff frequency.

$G \equiv \frac{V_{out}}{V_{in}} =$  gain

• RC case:  $|G| = \frac{1}{\sqrt{1 + (\omega RC)^2}} = \frac{1}{\sqrt{1 + (\omega/\omega_c)^2}}$  with  $\omega_c = \frac{1}{RC}$

In more detail :

- AMPLITUDE :  $\left| \frac{V_{out}}{V_{in}} \right| = |G| = \text{"attenuation"}$

can be expressed in decibels :


$$A_{dB} = -20 \log_{10} \left| \frac{V_{out}}{V_{in}} \right| = -10 \log_{10} \left| \frac{P_{out}}{P_{in}} \right| \quad \text{def-4.}$$

Interpret :  $A_{dB} = 10 \rightarrow$  power ( $\sim V^2$ ) delivered to load is reduced by a factor 10  
 $= 20 \rightarrow$  ... by a factor of 100

Low-pass filter :


$$A_{dB} = -10 \log_{10} \left( \frac{1}{1 + \omega^2/\omega_c^2} \right) \approx -20 \log_{10} \frac{\omega_c}{\omega}, \quad \omega \gg \omega_c$$
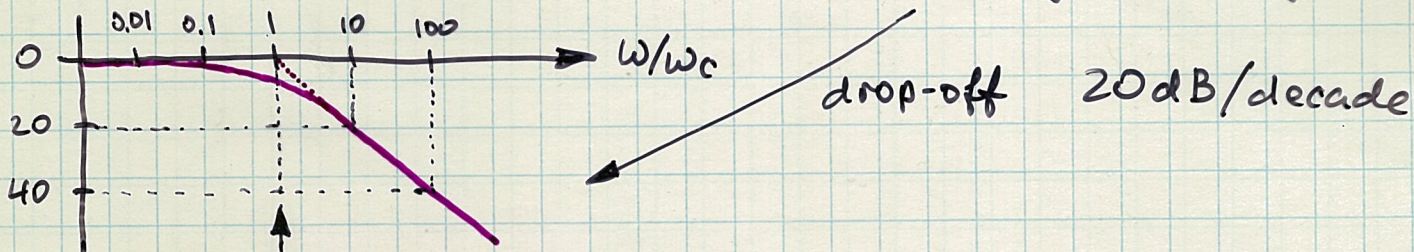
$$= -20 (\log_{10} \omega_c - \log_{10} \omega)$$



$\omega = \omega_c \Rightarrow A_{dB} = 20 \log_{10} \sqrt{2} \approx 3 \text{ dB} \leftarrow \text{"3dB point"}$

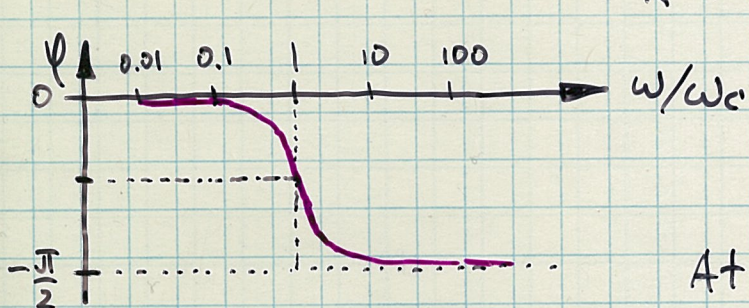- PHASE  $G = \frac{V_{out}}{V_{in}} = \frac{R^2 - j\omega RL}{R^2 + \omega^2 L^2} \Rightarrow \varphi = \arctan \left( \frac{-\omega L}{R} \right)$





$$\varphi = \arctan \frac{-\omega}{\omega_c}$$

true in both RL and RC circuits

At  $\omega = \omega_c : \varphi = -45^\circ$

# High-pass filters

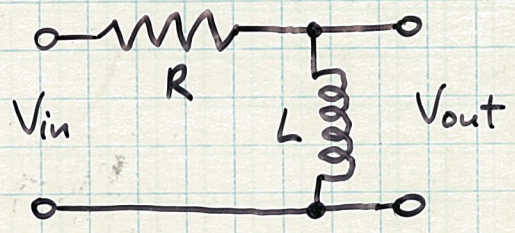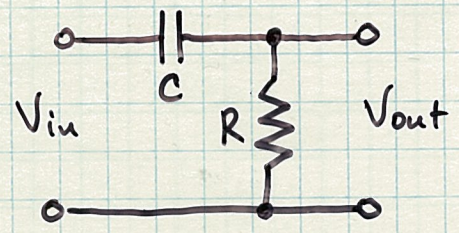


• RC case :

$$V_{out} = \frac{R}{R + \frac{1}{j\omega C}} V_{in} = \frac{\omega^2 R^2 C^2 + j\omega RC}{1 + \omega^2 R^2 C^2} V_{in}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{\omega RC}{\sqrt{1 + \omega^2 R^2 C^2}} = \frac{1}{\sqrt{1 + \frac{\omega_c^2}{\omega^2}}}, \quad \omega_c = \frac{1}{RC}$$

• RL case : same, with  $\omega_c = \frac{R}{L}$

⇒ the reverse of the low-pass case :

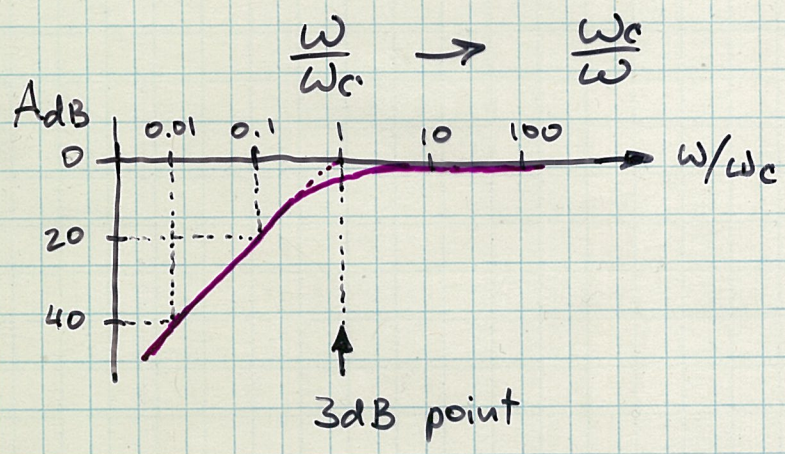


$\omega \ll \omega_c$  : A increases by 20dB per decade

$\omega \gg \omega_c$  :  $|G| \rightarrow 1$  ( $A = 0$  dB)

$\omega = \omega_c$  :  $A = -20 \log_{10} \frac{1}{\sqrt{2}} \approx 3$  dB

$$\varphi = \arctan \frac{\omega_c}{\omega}$$


$\varphi = +45^\circ$  at  $\omega = \omega_c$

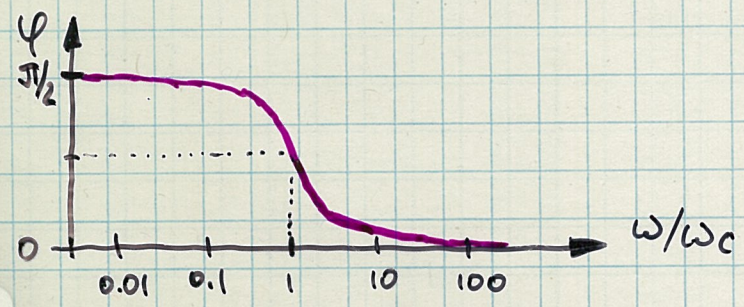

Note 1. phase shift inevitable if att-u varies with frequency

Note 2. independent filters in series: attenuations (dB) ADD

# Ex. Generalized Thevenin's equivalents

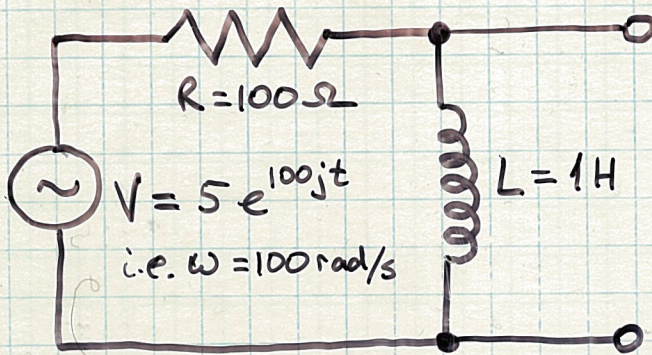

$$L = 1H @ \omega = 100 \text{ rad/s}$$



$$Z_L = 100j \Omega$$

A voltage divider :

$$V_L = 5 e^{100jt} \frac{100j}{100 + 100j} = 5 e^{100jt} \frac{j}{1+j} \frac{1-j}{1-j} = \frac{1+j}{2} 5 e^{100jt}$$

Magnitude :  $|\frac{5}{2}(1+j)| = \frac{5}{\sqrt{2}} = 3.54$

Phase :  $\varphi = \arctan 1 = 45^\circ = \frac{\pi}{4}$

$$\Rightarrow \underline{V_{oc.}} = V_L = 3.54 e^{j\pi/4} e^{100jt} = \underline{3.54 e^{j(100t + \pi/4)}}$$

Thevenin's equivalent :  $V_{Th.} = V_{oc.}$

$$I_{sc.} = \frac{V}{R} = \frac{5 e^{100jt}}{100}$$

↙ L is shorted out

$$\Rightarrow \underline{Z_{Th.}} = \frac{V_{oc.}}{I_{sc.}} = \frac{\frac{1+j}{2} 5 e^{100jt}}{\frac{5 e^{100jt}}{100}} = 100 \frac{1+j}{2} = 50 + 50j \Omega$$


Represent  $Z_{Th}$  as  $R_T + j\omega L_T$  : @  $\omega = 100$

$$R_T = 50 \Omega$$


$$L_T = 0.5 H$$

⇒ Equivalent circuit :

$$V_T = 3.54 e^{j(100t + \pi/4)}$$

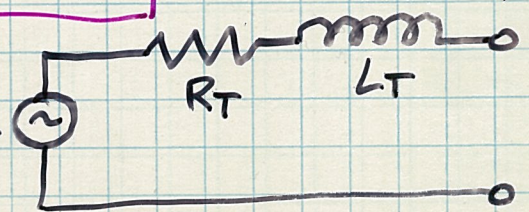
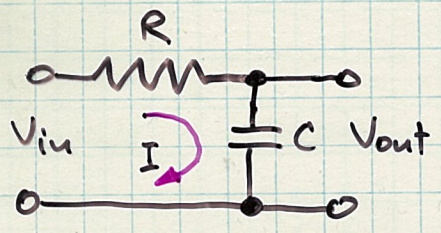
# Integrators & differentiators - another use of RC circuit




KCL:  $\frac{V_{in} - V_{out}}{R} = C \frac{dV_c}{dt} = V_{out}$

if  $V_{out} \ll V_{in}$ :  $V_{out} \approx \frac{1}{RC} \int V_{in} dt$

RC integrator.

Note: RL integrator is also possible, but capacitors are smaller, cheaper, and more ideal

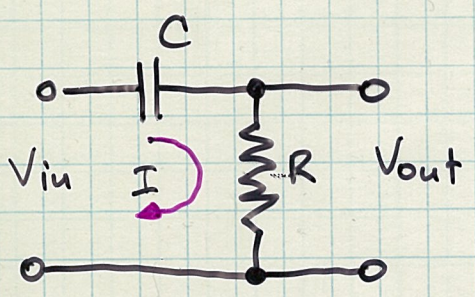Note:  $V_{out}$  small is equivalent to  $\tau$  small compared to the time constant of the circuit.




KCL:  $C \frac{d}{dt}(V_{in} - V_{out}) = \frac{V_{out}}{R}$

$V_{out} \ll V_{in} \Rightarrow V_{out} \approx RC \frac{dV_{in}}{dt}$

RC differentiator

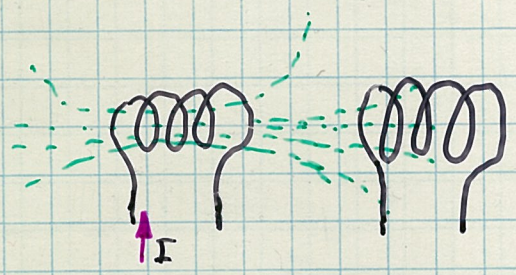
## Transformers

= two inductors placed close enough so that one intercepts [some of] the magnetic flux of the other:



E.g.

most of flux shared by both windings

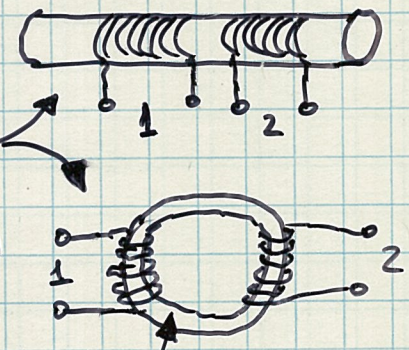

(95% typical)

iron core

Flux in primary  $\Phi = \int \frac{V_1}{N_1} dt$  ← turns of primary

Voltage on secondary (Faraday's Law):


$$V_2 = N_2 \frac{d\Phi}{dt}, \quad N_2 = \text{turns of secondary}$$

$$\Rightarrow \frac{V_2}{V_1} = \frac{N_2}{N_1} \begin{cases} \text{"step-up", } N_2 > N_1 \\ \text{"step-down", } N_2 < N_1 \end{cases}$$

Voltage ratio = turns ratio, independent of frequency, for ideal transformers.

Real transformers:  $I_1 = \frac{V_1}{j\omega L_1}$  ← this limits the low frequency.

### Power transfer

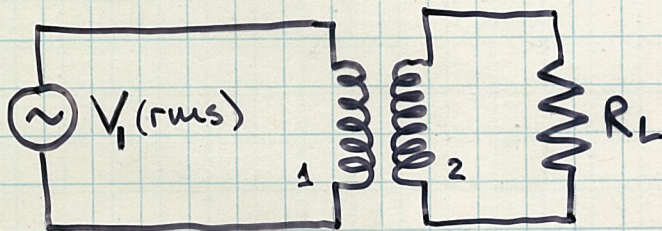

rms voltage across  $R_L$

$$\text{is } V_2 = \frac{N_2}{N_1} V_1$$

$$\Rightarrow \text{Power dissipated by } R_L: P = \frac{V_2^2}{R_L} = \frac{N_2^2 V_1^2}{N_1^2 R_L}$$

Ideal transformer does not dissipate power, so the current in primary must be:

$$I_1 = \frac{P}{V_1} = \frac{N_2^2 V_1}{N_1^2 R_L} = \frac{V_1}{\frac{N_1^2}{N_2^2} R_L} = \frac{V_1}{R_{eq}}, \quad \boxed{R_{eq} = \frac{N_1^2}{N_2^2} R_L}$$

i.e. the source thinks it is connected to  $R_{eq}$ .

Generalize: also true for  $\boxed{Z_{eq} = \frac{N_1^2}{N_2^2} Z_L}$

To maximize power transfer, use a transformer to match impedances  $Z_{source} = Z_{eq}$ .