
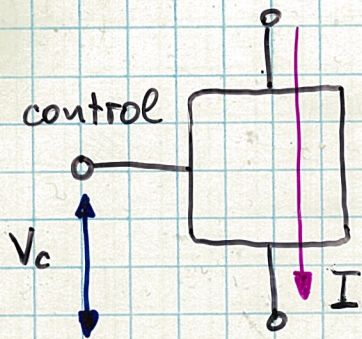


General amplifier theory.

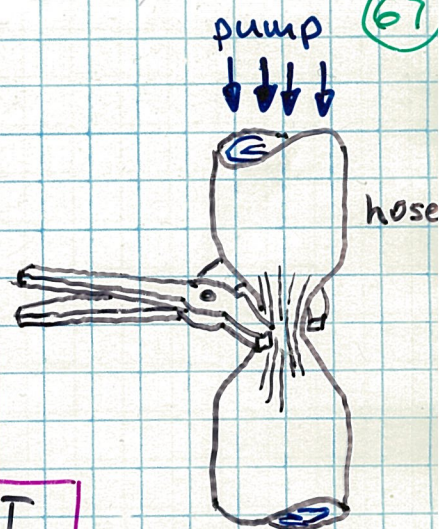

small V_c
controls large I
(I supplied by
an external source)



Mutual transconductance


$$g_m \equiv \frac{\Delta I}{\Delta V_c}$$

The control device can be a transistor or a vacuum tube (British: "valve").

Typical use

need also:

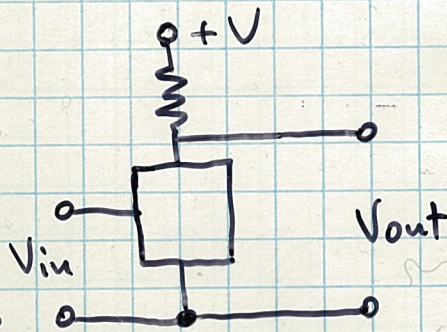- coupling C
- bias voltages
- in/out impedance matching



= Amplifier


$$G_v = \frac{\Delta V_{out}}{\Delta V_{in}}$$

only signals, no biases or offsets

Assuming that we can take care of the technical details - why use amplifiers?



- detect weak signals
- use as controllers (small $\Delta V_{in} \rightarrow$ large ΔV_{out})
- perform mathematical operations (op-amps)

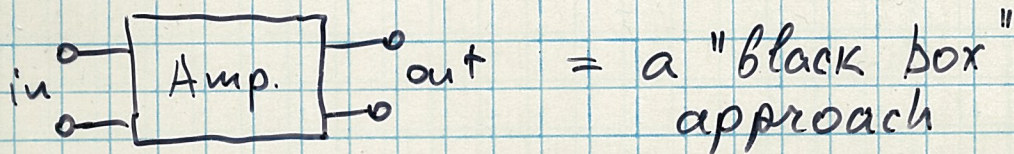
Some common features of all active circuit elements.



Operational amplifiers

Basic terminology


- Gain (voltage or current) $G_v = \frac{V_{out}}{V_{in}}$ \rightarrow signals only
- G , in general, is a complex number, i.e. there may be a change in phase as well as amplitude
- input impedance: how  loads up the source
- output impedance:  $Z = Z_{Th}$ of the "black box"
- $G = G(\omega)$, frequency response of an amp
- $|G|$ may be $< 1 \Rightarrow$ attenuators

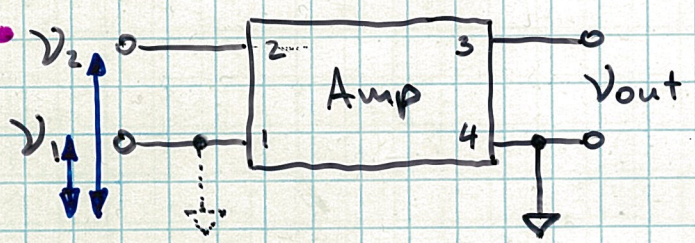

In general, 1 & 4 are not necessarily the same (not referenced to ground)

$\Rightarrow V_{out} \propto (V_2 - V_1)$

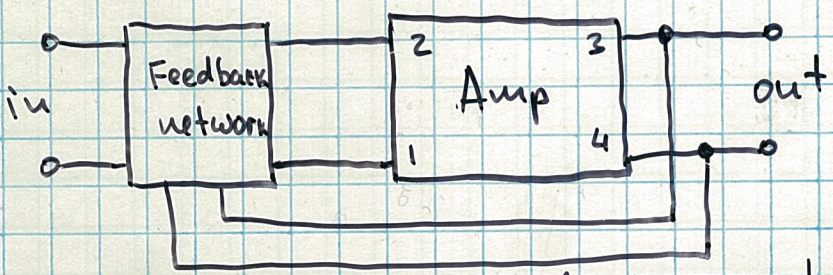\Rightarrow difference amplifier
differential inputs




Part of the output diverted back to input — feedback

negative feedback: higher output suppresses further increases

positive feedback: higher output stimulates further increases

Ex. a typical op-amp (741)

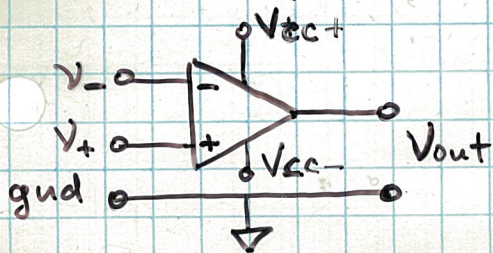


$V_+ > V_- \Rightarrow V_{out}$ positive
 $V_- > V_+ \Rightarrow V_{out}$ negative

typical $R_{in} \sim 2M\Omega$ $R_{out} \sim 75\Omega$
 $V_{cc+} \approx +15V$ $V_{cc-} \approx -15V$

open loop gain (no feedback) $A \sim 103dB$ (nominal)

frequency response : flat ϕ (DC) — 100Hz
 decreases to $A \sim 1$ at $\sim 1MHz$

The importance of feedback

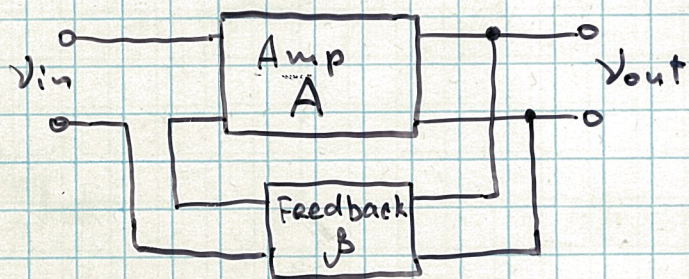

β = feedback fraction


$$V_{out} = A (V_{in} + \beta V_{out})$$

$$\Rightarrow V_{out} = \frac{A}{1 - \beta A} V_{in}$$

For $\beta A \gg 1$: $V_{out} \approx -\frac{1}{\beta} V_{in}$ independent of A!
 (i.e. large A)

i.e. the gain of the circuit is completely determined by the feedback network, not by op-amp itself.
 \Rightarrow closed loop gain

Ex.

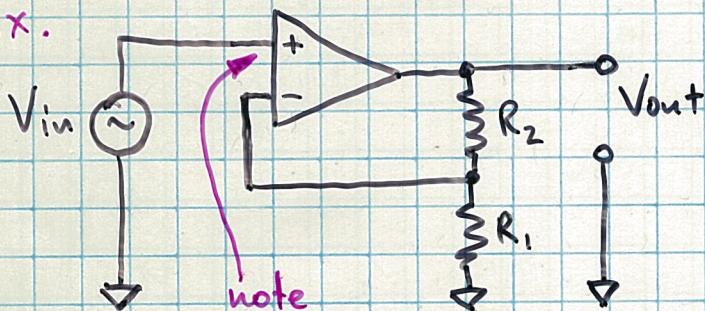

Voltage divider provides the feedback voltage

$$V_{out} \frac{R_1}{R_1 + R_2}$$

i.e. $\beta = -\frac{R_1}{R_1 + R_2}$


"minus" because connected to the - input of the op-amp

$$\Rightarrow V_{out} = -\frac{1}{\beta} V_{in} = -\frac{R_1 + R_2}{R_1} V_{in}$$

Ideal and real op-amps

Ideal op-amp value
 \emptyset

Input offset voltage

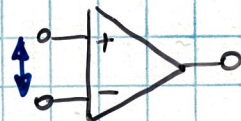

In a real op-amp, the two inputs are not perfectly balanced. I.O.V. is the voltage needed at the input to bring the output to zero.

741: 2mV, slightly temperature-dependent, 3 μ V/ $^{\circ}$ C

In some op-amps there are extra leads to attach an external balance potentiometers to null the offset voltage

Input bias currents



\emptyset

origin: gate leakage currents of FETs, etc.

741: 0.1 μ A. I.b.c. are quite sensitive to temperature changes, $\sim \times 2/10^{\circ}$ C. The difference of the two i.b.c. is input offset current

Input resistance = $\frac{i.o.v.}{i.o.c}$ can be $\leq 10^{14} \Omega$ ∞

Output resistance: limits the max power \emptyset



that an op-amp can dissipate ($= V_{out}^2 / R_{out}$)

741: 75 Ω ; some can be $\leq 1 \Omega$ (high-power)

Frequency response

not very good!

for an op-amp in an open-loop config.

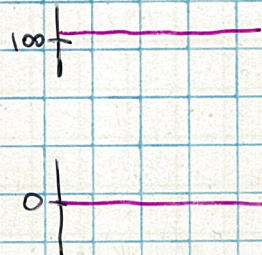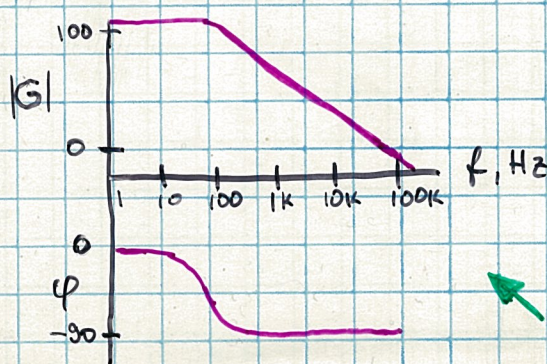


← "Bode plot"

IC op-amp LF351


- Input offset voltage 2mV
- Input bias current 50pA
- $R_{in} \approx 10^{12} \Omega$
- $A = 100 \text{ dB}$ (open loop)

Noninverting input (+) V_+


Inverting input (-) V_-

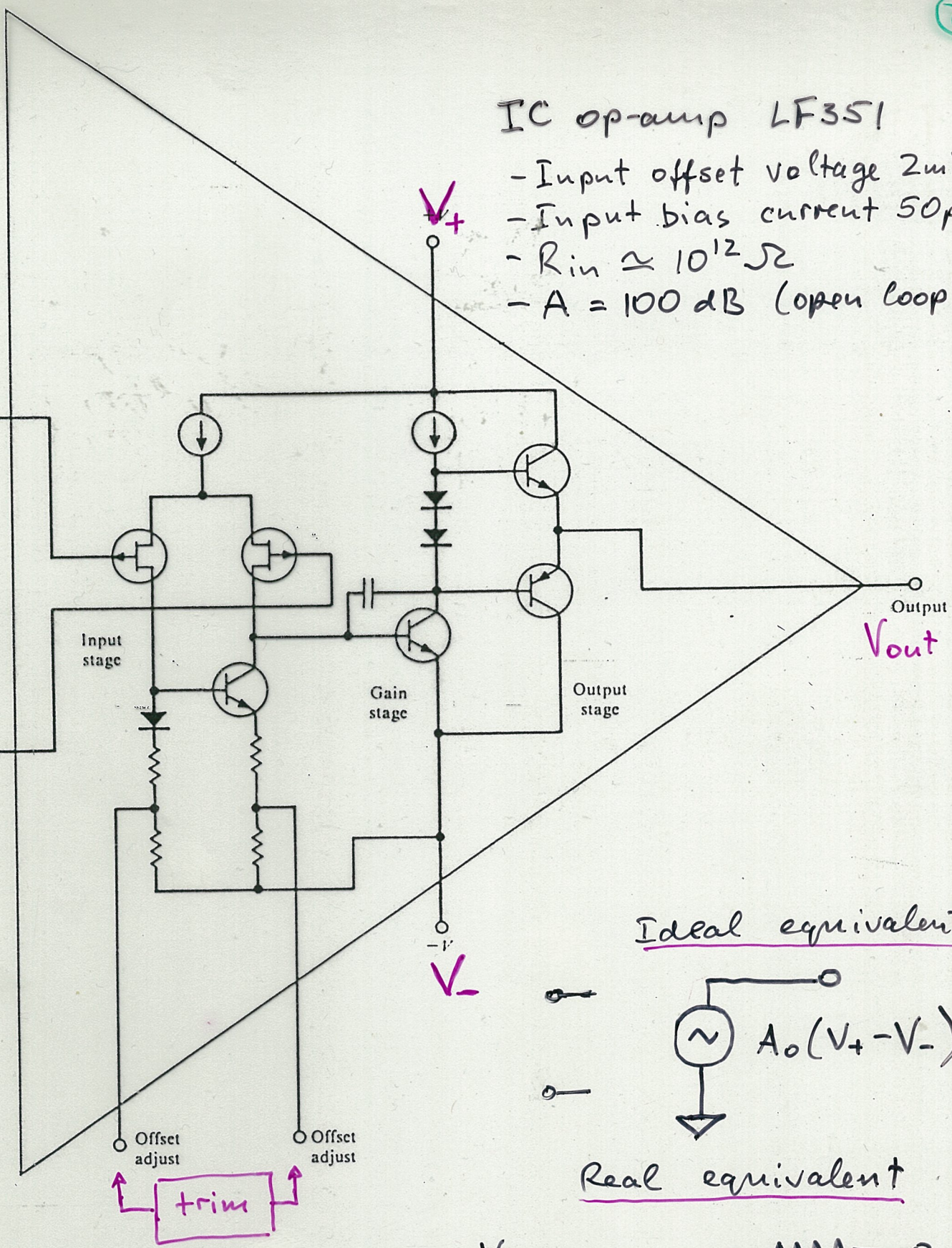


Ideal equivalent

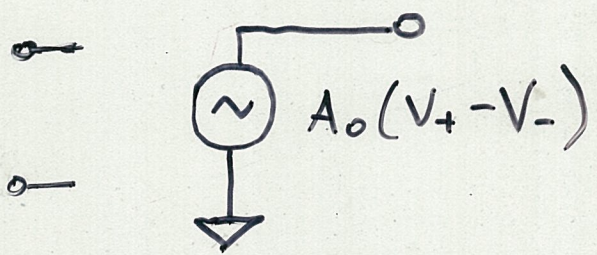

Real equivalent

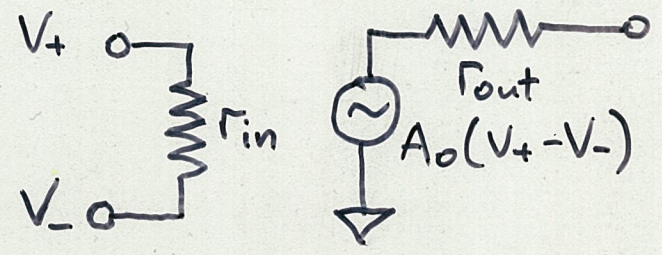

Analyzing op-amp circuits

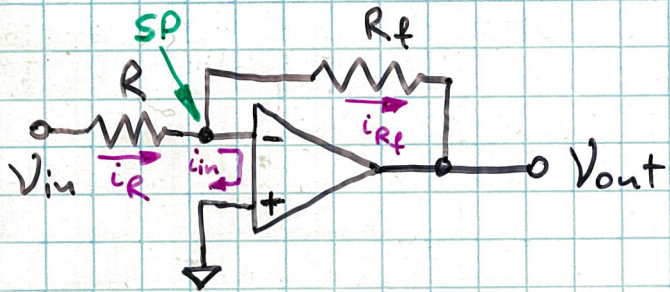

Principle: make simplifying assumptions & treat an op-amp as an ideal device. Deal with imperfections later if interested.

① Assume $A = \infty$.

For a circuit with feedback, $\frac{V_{out}}{V_{in}} = \frac{A}{1 - \beta A}$

E.g. $A \approx 10^{+5}$, $\beta = -0.01 \Rightarrow \frac{V_{out}}{V_{in}} \approx -99.9$

+10%: $A \approx 1.1 \cdot 10^{+5}$, $\beta = -0.01 \Rightarrow \frac{V_{out}}{V_{in}} \approx -99.89$ (-0.1%)

Closed loop gain is determined mostly by β , not A

If $A = \infty$ then $V_+ - V_- = \frac{V_{out}}{A} = \phi$, i.e.

$V_+ = V_-$ \leftarrow virtual ground approximation
 (-ve input is at ground, see above)

! op-amp with a negative feedback tries to maintain zero voltage across its + & - inputs.

② $i_{in} = \phi \Rightarrow R_{in} = \infty$

Input bias current is zero. \Rightarrow ! op-amp draws no current.

Apply KCL at the summing point (SP):

$$i_R - i_{in} = i_{Rf}, \text{ with } i_{in} = \phi \Rightarrow i_R = i_{Rf}$$


Since SP is at virtual ground, $i_R = V_{in}/R$

$$i_{Rf} = -V_{out}/R_f$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = G_{os} = -\frac{R_f}{R}$$


\leftarrow inverting amp.

Non-inverting amplifier

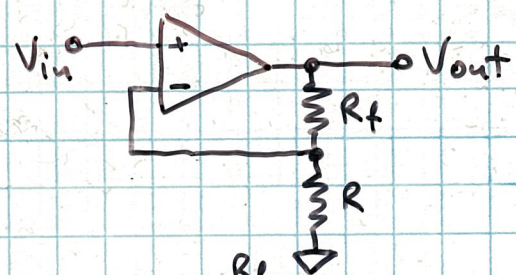


$$G_V = \frac{R_f + R}{R} = 1 + \frac{R_f}{R}$$

Inverting amplifier

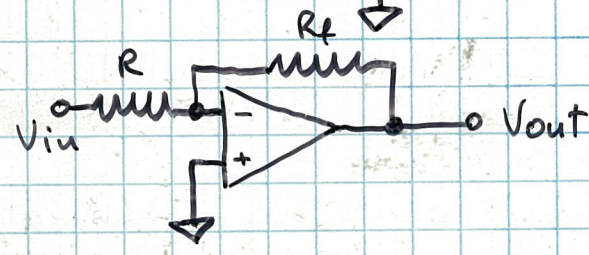

$$G_V = -\frac{R_f}{R}$$

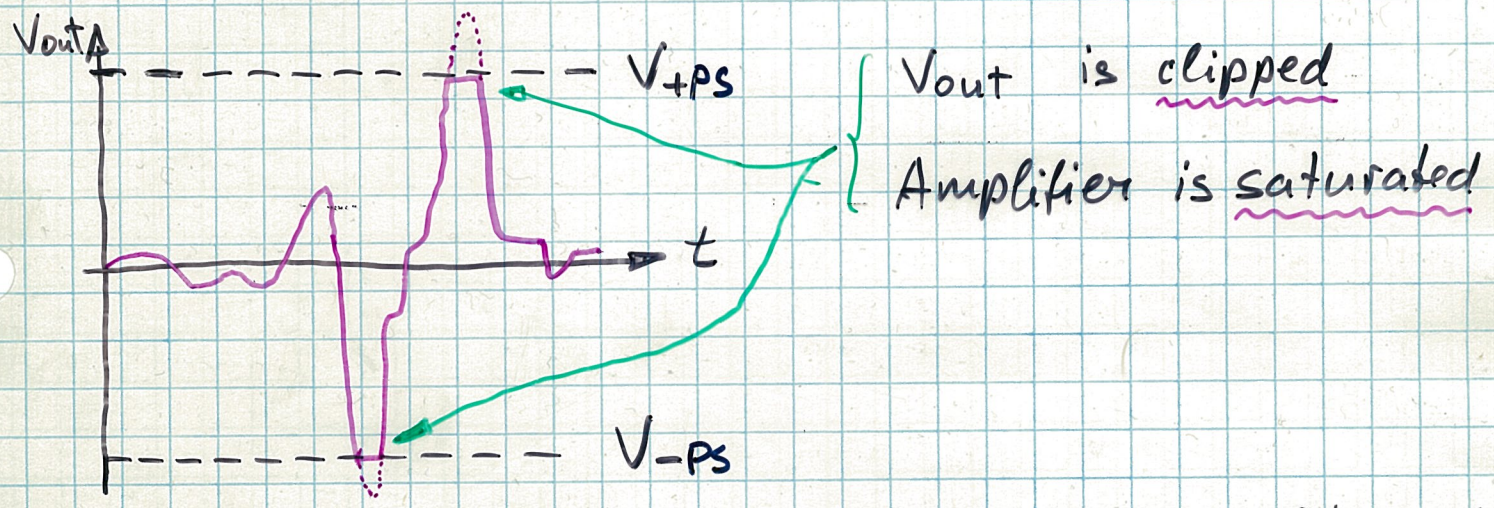- These two assumptions may break down when the desired V_{out} exceeds the power supply voltages:




- Another restriction is the max values of R 's that are practical: as we reach ~ 10 's $M\Omega$, the value of the resistor becomes comparable to the leakage resistance of the surrounding insulators. So, to get gains of ~ 100 we need to keep R down

$$100 \sim \frac{R_f}{R}, \quad R_f \leq 10M\Omega \Rightarrow R \leq 100k\Omega$$

And $R =$ input resistance of the above inverting amp circuit (more complex in non-inverting case, $R_{in} \propto \frac{R}{R+R_f}$) i.e. in practice input resistance $< \infty$

A catalog of op-amp circuits

voltage follower

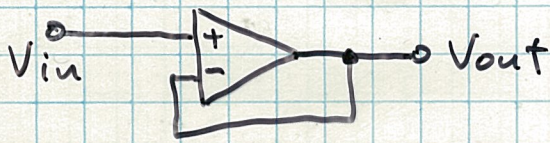


Non-inv. amp with $R_f = \phi$

$$\Rightarrow G_v = 1 + \frac{R_f}{R} = 1$$

$$\Rightarrow \boxed{V_{in} = V_{out}}$$

useful as impedance transformer. Note that the power gain need not be 1 \Rightarrow a buffer

summing amplifier

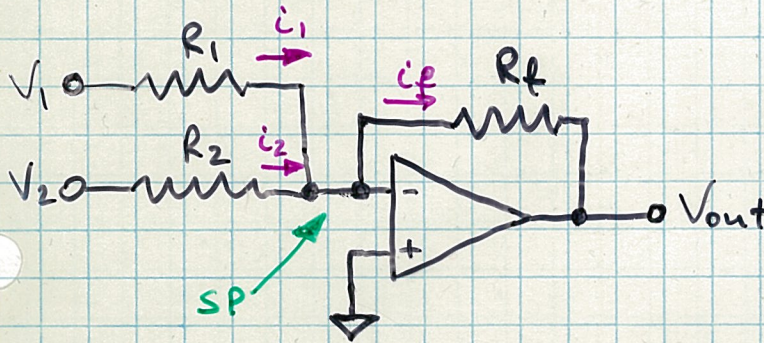

1) KCL at Summing Point (SP)

$$\Rightarrow i_1 + i_2 = i_f \text{ (op-amp draws no current!)}$$

2) Virtual ground: $V_+ = V_- = \phi$

$$\Rightarrow i_1 = \frac{V_1}{R_1} \quad i_2 = \frac{V_2}{R_2} \quad i_f = \frac{-V_{out}}{R_f}$$

$$\Rightarrow V_{out} = -\frac{R_f}{R_1} V_1 - \frac{R_f}{R_2} V_2$$

$$= -(V_1 + V_2)$$


\leftarrow a weighted sum

\leftarrow for $R_1 = R_2 = R_f$

! virtual ground at \Rightarrow inputs do not interact

N.B. only works in an inverting configuration!

current-to-voltage converter

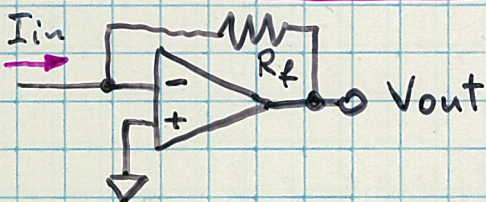


At summing pt: $I_{in} + \frac{V_{out}}{R_f} = \phi$

$$\Rightarrow \underline{V_{out} = -R_f I_{in}}$$

N.B. the above summing amplifier can be viewed as an adder of currents (just omit the R's)

difference amplifier

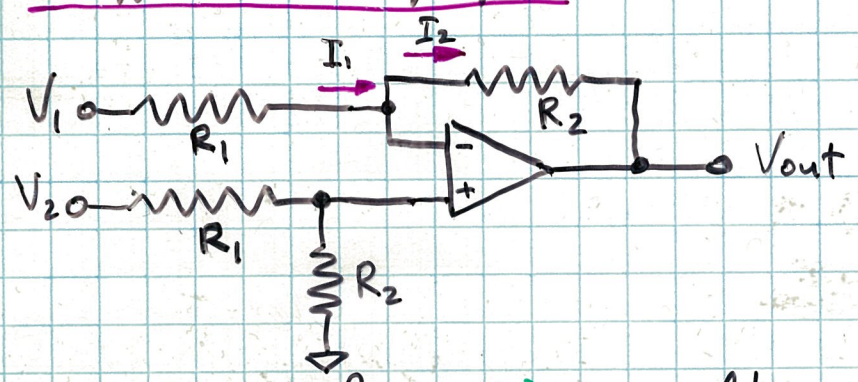

$$V_{out} = \frac{R_2}{R_1} (V_2 - V_1)$$

1. $V_+ = V_2 \frac{R_2}{R_1 + R_2}$ (*) (a voltage divider)

2. virtual ground approximation: $V_- = V_+$


3. $\Rightarrow I_1 = I_2 \Rightarrow \frac{V_1 - V_-}{R_1} = \frac{V_- - V_{out}}{R_2}$

$\Rightarrow \frac{V_1}{R_1} - \frac{V_+}{R_1} = \frac{V_+}{R_2} - \frac{V_{out}}{R_2}$ (**)


4. Solve (*) & (**) to eliminate V_+ and get the above result

In practice: careful matching of the resistors is needed

Ex.1. using differential amplifiers to eliminate noise.

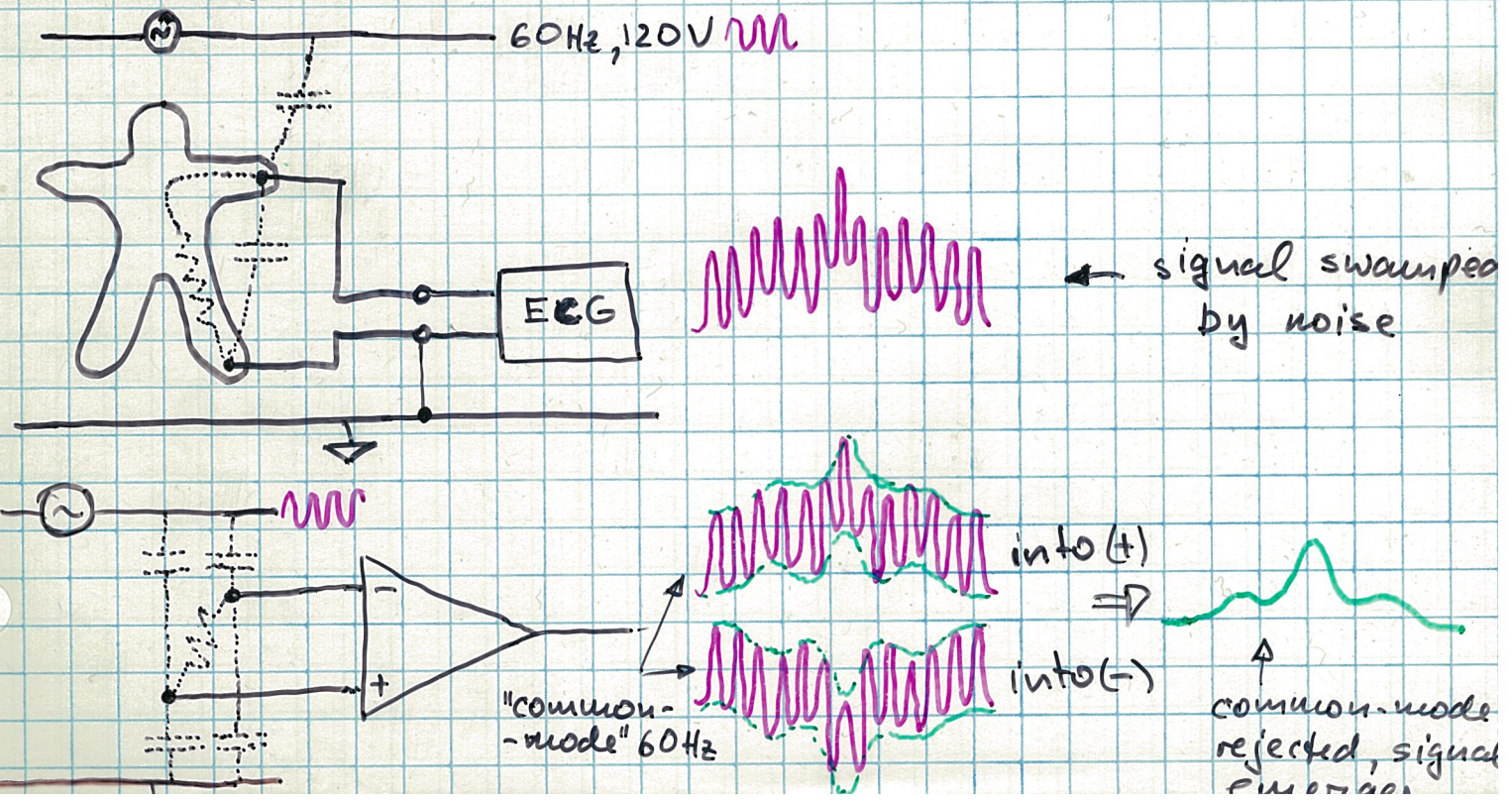

Ex 2. Analog arithmetics

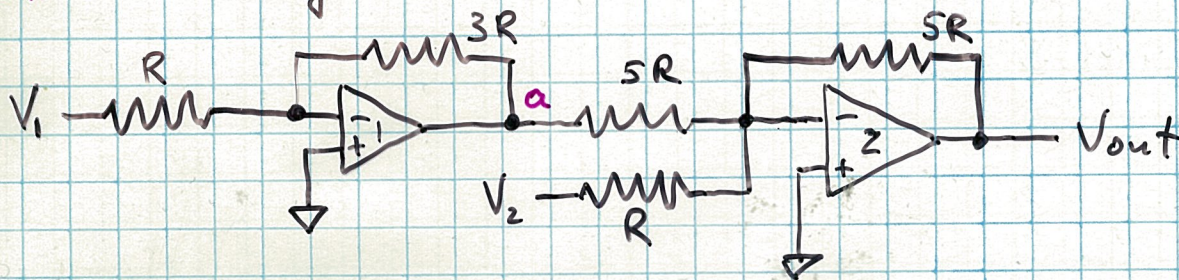


1. Amp 1: inverting amplifier, gain = 3

$\Rightarrow V_a = -3V_1$

2. Amp 2: summing amplifier

$\Rightarrow V_{out} = -\left(\frac{5R}{5R} V_a + \frac{5R}{R} V_2\right) = -V_a - 5V_2 = 3V_1 - 5V_2$

the integrator

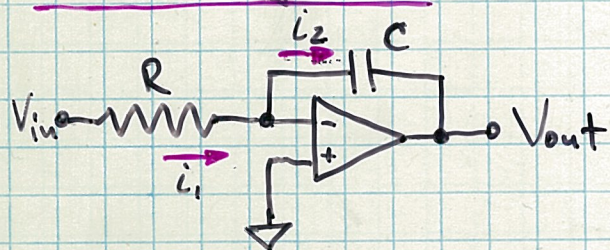


KCL at S.P.: $i_1 = i_2$

$\Rightarrow \frac{V_{in}}{R} = -C \frac{dV_{out}}{dt}$

$\Rightarrow V_{out} = -\frac{1}{RC} \int_0^t V_{in} dt + const$

We assume $const = V_{out}(t=0) = \phi$

the differentiator

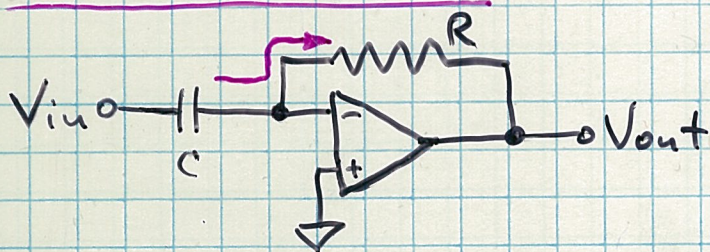

Again, at S.P.:

$-\frac{V_{out}}{R} = C \frac{dV_{in}}{dt}$


$\Rightarrow V_{out} = -RC \frac{dV_{in}}{dt}$

Note: for a sine wave, \int or $\frac{d}{dt}$ brings out a frequency dependence:

- integrator: $V_{out} = V_{in} \frac{j}{R\omega C} \rightarrow$ low-pass filter

- differentiator: $V_{out} = V_{in} j\omega RC \rightarrow$ high-pass filter

logarithmic amplifier

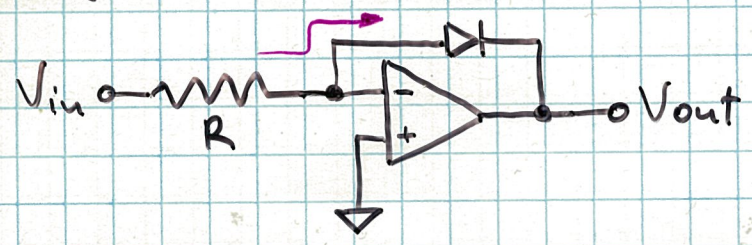

Diode has an exponential voltage-current dependence


$$\Rightarrow \frac{V_{in}}{R} = B e^{V_{out}/\alpha}$$

B, α = const.

$$[\alpha] = V \quad [B] = A$$

$$\Rightarrow V_{out} = \alpha \ln \frac{V_{in}}{RB}$$

exponential amplifier

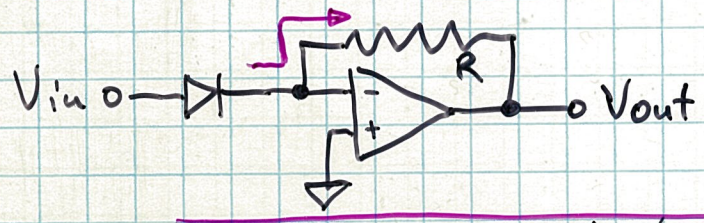


interchange R and diode:

$$B e^{V_{in}/\alpha} = -\frac{V_{out}}{R}$$


$$\Rightarrow V_{out} = -RB e^{V_{in}/\alpha}$$

Combining op-amp "building blocks" - analog computing

multiplication

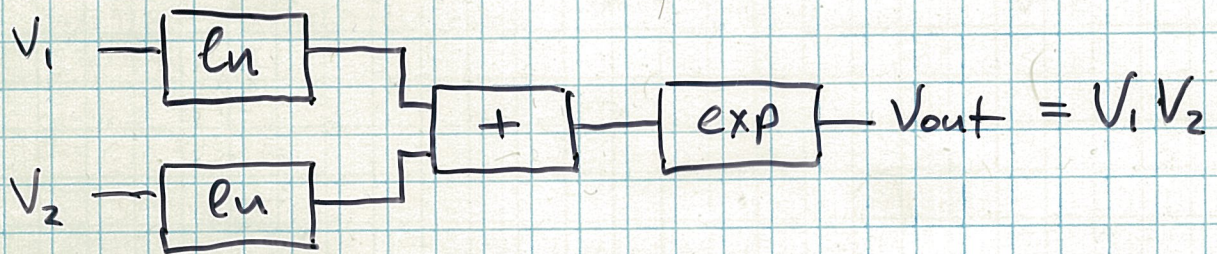


square root

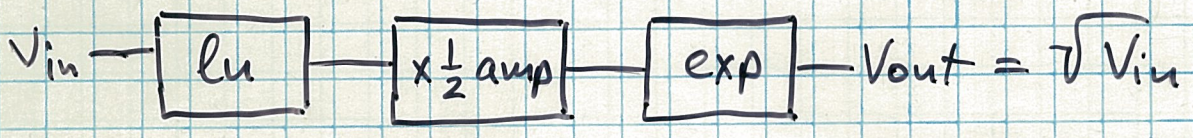

differential equations

in principle:

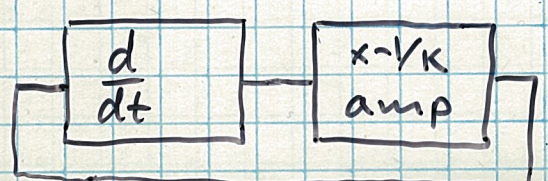

$$V = -\frac{1}{k} \frac{dV}{dt}$$


$$\text{or } \dot{V} + kV = 0$$

in practice:

used to solve differential equations by setting the IC's

instrumentation amplifier

useful in many measuring instruments

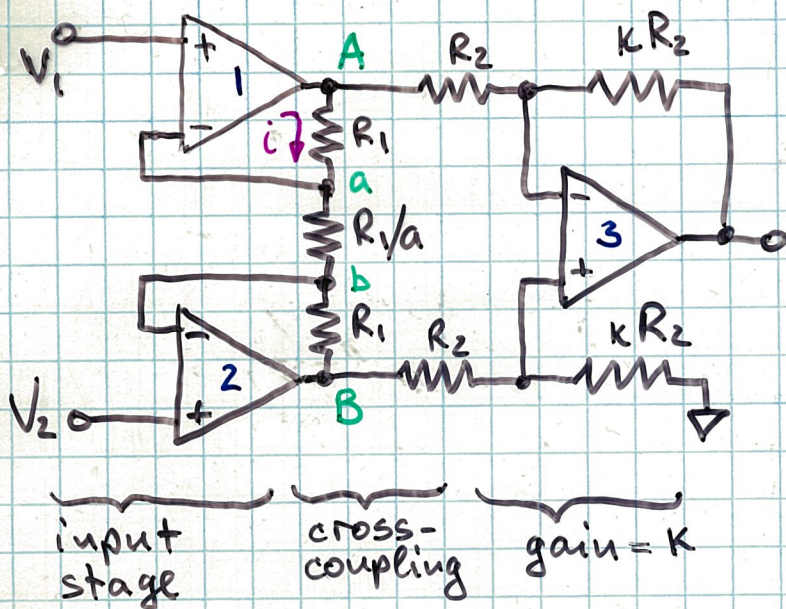

① input stage is a couple of voltage followers: buffer stage to get high input impedance

② cross-coupling: a clever way to make the two input channels track each other:

$$\begin{aligned} V_A &= V_1 \\ V_B &= V_2 \end{aligned} \Rightarrow i = a(V_1 - V_2) / R_1 \quad (\text{op-amps themselves draw no current})$$

$$\Rightarrow \begin{cases} V_A = V_1 + a(V_1 - V_2) \\ V_B = V_2 - a(V_1 - V_2) \end{cases}$$

$$\Rightarrow \left. \begin{aligned} A_{\text{difference}} &= \frac{V_A - V_B}{V_1 - V_2} = 1 + 2a \\ A_{\text{common-mode}} &= \frac{V_2(V_A + V_B)}{V_2(V_1 + V_2)} = 1 \end{aligned} \right\} \begin{array}{l} \text{Not sensitive} \\ \text{to precision} \\ \text{matching of } R_1 \text{'s} \end{array}$$

→ with reasonable R's can easily obtain common-mode rejection ratio.


$$\text{CMRR} \equiv \frac{A_{\text{diff}}}{A_{\text{c.m.}}} = \frac{1 + 2a}{1} \sim 10 \text{ to } 1000$$

in the input stage alone! (x CMRR of op-amp 3)



! || the above circuit as a whole is a much better
• || op-amp: high R_{in} , high CMRR.

Mathematical aside: signal modulation

Signal:
 $A_s \cos \omega_s t$

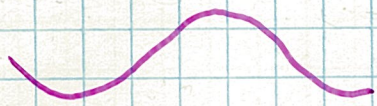


Carrier:
 $A_c \cos \omega_c t$

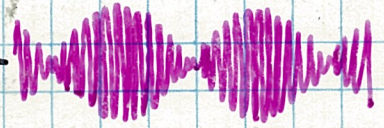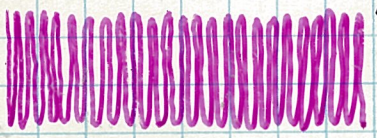

$$A_c \cos \omega_c t * A_s \cos \omega_s t = \frac{A_c A_s}{2} [\cos(\omega_c - \omega_s)t + \cos(\omega_c + \omega_s)t]$$

In frequency domain:

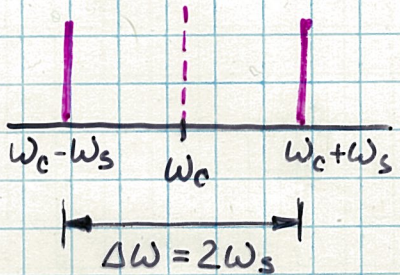

Must be reversible to be useful!


=> Demodulation:

Modulated carrier

$$A_c \cos \omega_c t * A_s \cos \omega_s t$$

Reference

$$A_c \cos \omega_c t$$

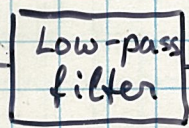

$$\frac{A_c A_s}{2} \cos \omega_s t$$

$$\frac{A_c^2 A_s}{2} \cos \omega_s t + \frac{A_c^2 A_s}{2} \cos \omega_s t \cos 2\omega_c t$$

high freq.


=> can encode and recover the original signal

Ex.1. AM radio


Ex.2. heterodyne amplification

(amplify at a frequency where it is easier!)

lock-in amplifier

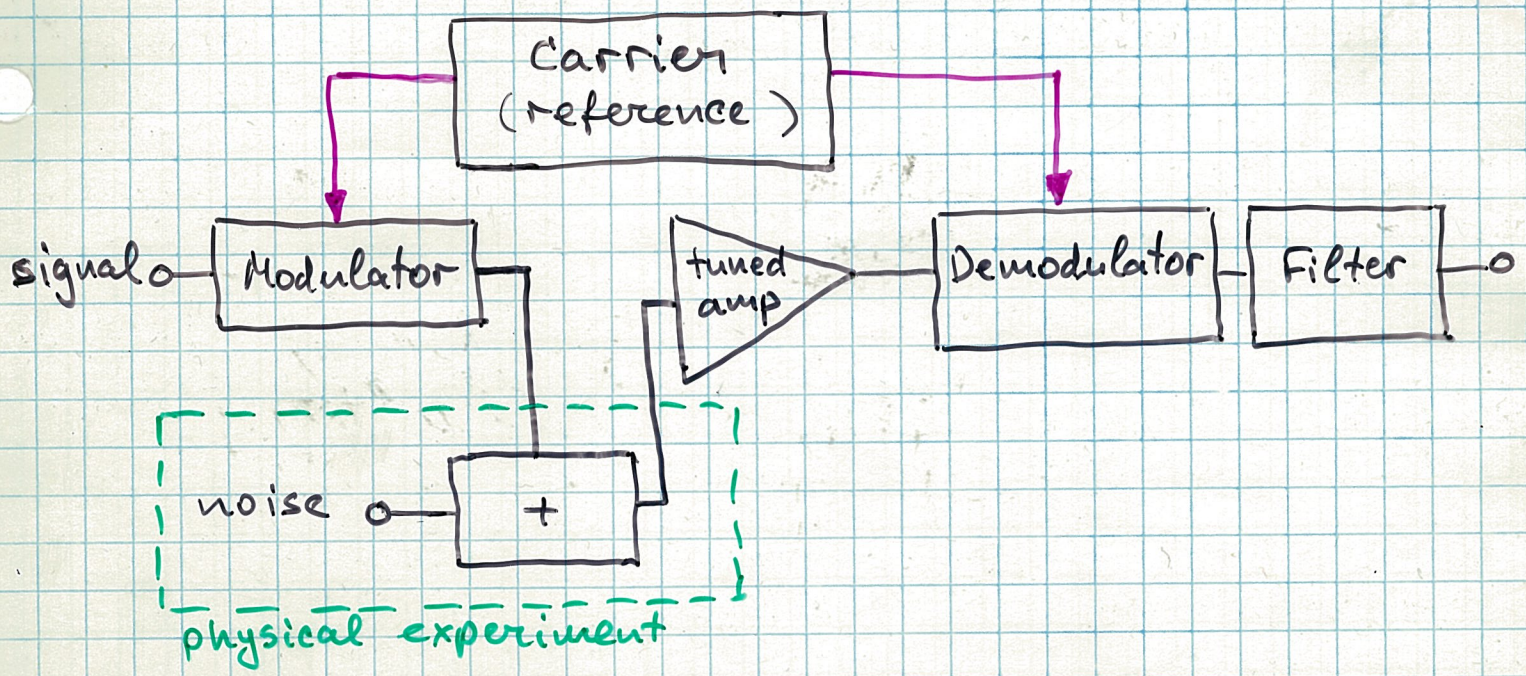

- "tag" the signal by carrier
 - put the modulated signal to use (e.g. send light to probe optical properties)
 - the signal emerges "buried" in the noise
 - use a "phase-sensitive detector", i.e. treat signal during the +ve half of the carrier wave differently from the signal during the -ve half. \Rightarrow de-modulate.
- Those components that do not vary with carrier (noise) will get averaged to zero; those that vary in-phase with carrier, will add up.
- \Rightarrow extract the "buried" signal

Note: the carrier need not be a sine wave!
 E.g.  \Rightarrow lends itself to "digital" (on/off) versions of lock-in amplifiers

Note: distinguished history of lock-in detection in physics

See: Am. J. Phys
59: 569-572, 1991

Note: "signal" & "noise" have same period \Rightarrow overlapping "noise" frequency spectra \rightarrow

Note: can modulate by a square wave, too!
i.e. "chop" the signal

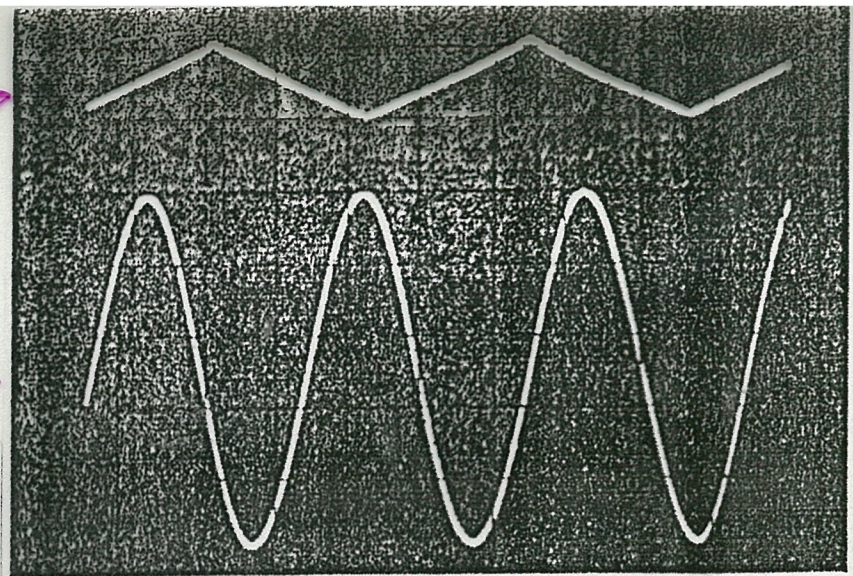
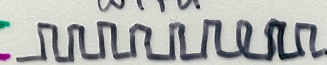

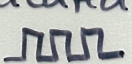
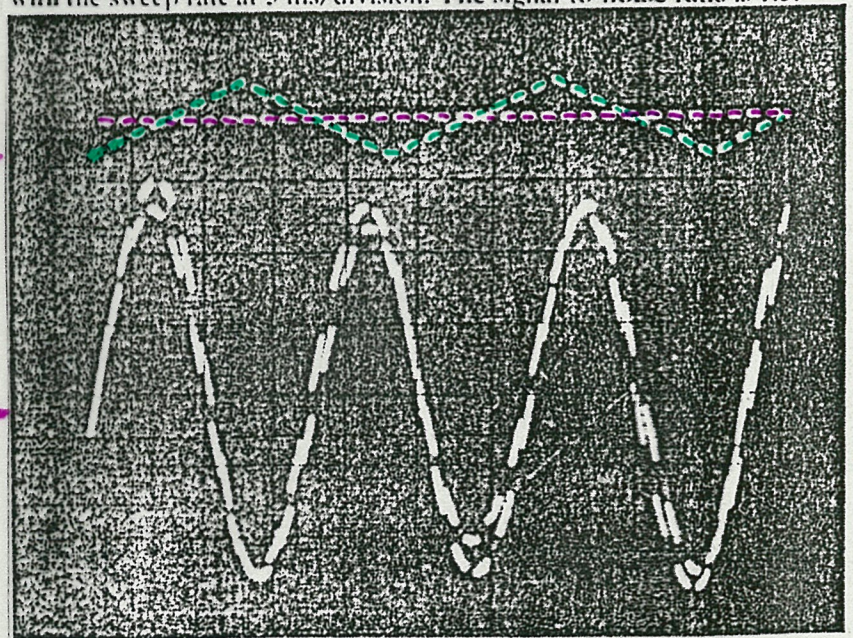


Fig. 4. Signal (upper trace) and "noise" (lower trace), shown at the inputs to the circuit of Fig. 2. Both traces are displayed at 1 V/division, with the sweep rate at 5 ms/division. The signal-to-noise ratio is 1:5.

signal modulated with 

Note: signal is buried by noise; little evidence of  (triangular wave)

signal+noise modulated with 



ignore \rightarrow

demodulated signal \rightarrow

