

(3) ① Prove the following Boolean equalities

$$A + \bar{A}B = A + B ; AB + \bar{A}C = AB + BC + \bar{A}C ; AB + \bar{A}\bar{B} + \bar{A}B = A + B$$


(3) ② Reduce to the simplest forms

$$ABCD + \bar{A}\bar{B}\bar{C}D ; AB + \bar{A}C + \bar{A}\bar{B}C(AB + C) ; A + B(\bar{C} + \overline{\overline{DE}}) ;$$

(4) ③ Implement the following using only NAND gates

$$AB + \bar{A}\bar{B} + \bar{A}\bar{B} + \bar{A}\bar{B} ; (AB + C)(AB + D) ; (\bar{A}\bar{B})(\bar{A}B) + AB ; (1 + B)(ABC)$$

(2) ④ Implement AND, OR, NAND using only NOR gates

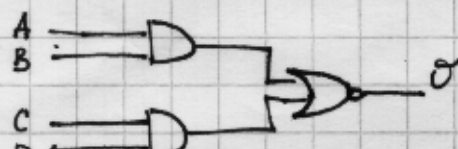(3) ⑤  This is the so-called AND-OR-Invert gate (AOI). Develop its truth table


(3) ⑥ Convert the following numbers into decimal

$$110101_2 \quad 754_8 \quad A10E_{16}$$

(4) ⑦ Convert the following numbers into binary

$$67_{10} \quad 3625_{10} \quad 635_8 \quad 8FE_{16}$$

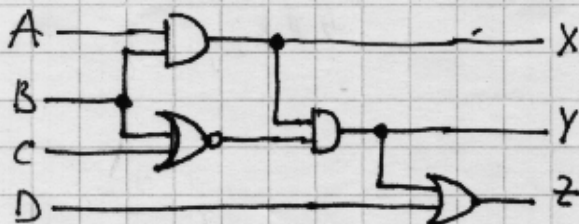(3) ⑧ Derive Boolean expressions to describe the operation of this circuit. Minimize these expressions by algebraic manipulation and hence simplify the circuit



(5) ⑨ Complete all Exercises - For - The - Students (EFTSs) in Section 14: pp. 14-9, 14-10, 14-14, 14-21