

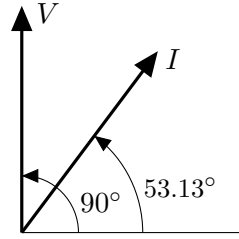


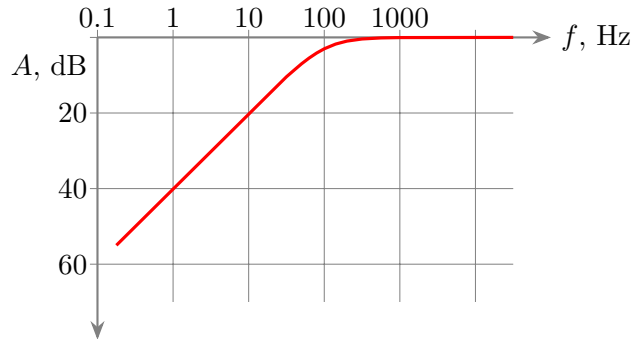- (4) 1. Shown is the voltage-current phasor diagram for a two-element series circuit at angular frequency 300 rad/s. What are the two elements and their values if the phasor magnitudes are 200 V and 20 A?




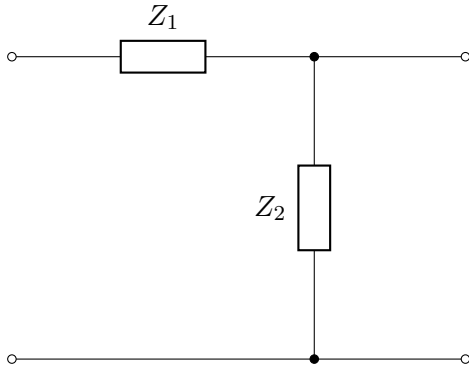- (4) 2. The circuit shown has the following attenuation factor:



- (a) What type of circuit is this?
- (b) What circuit components Z_1 and Z_2 could you choose? Is there more than one way to obtain such attenuation factor A ?
- (c) Sketch the phase φ of V_{out} , relative to V_{in} , as a function of frequency f .

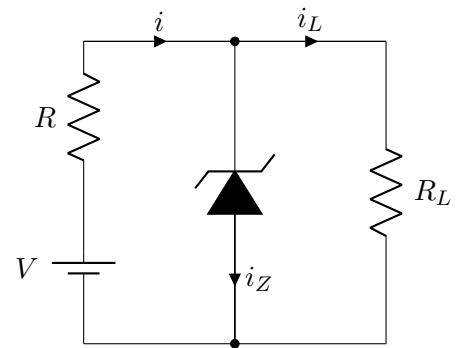- (4) 3. This is a *voltage regulator* circuit, providing a constant voltage to the load R_L . Here, $R = 1 \text{ k}\Omega$ and $V = 25 \text{ V}$. The maximum rated current through the 15-V Zener diode is 150 mA.



- (a) Over what range of R_L values is the regulator useful?
- (b) For a constant $R_L = 5.0 \text{ k}\Omega$, over what range of input voltages V can regulation be achieved?

- (2) 4. For *voltage* gains of 45 dB, 2.3 dB, -5.4 dB, calculate the multiplicative gain values, *i.e.* $|V_{out}/V_{in}|$. Repeat, interpreting the values as *power* gains.

- (3) 5. Use $R_f = 1000 \Omega$ and calculate the values of R_1, R_2, R_3 such that

$$V_{out} = -(V_1 + V_2 - V_3)$$

